

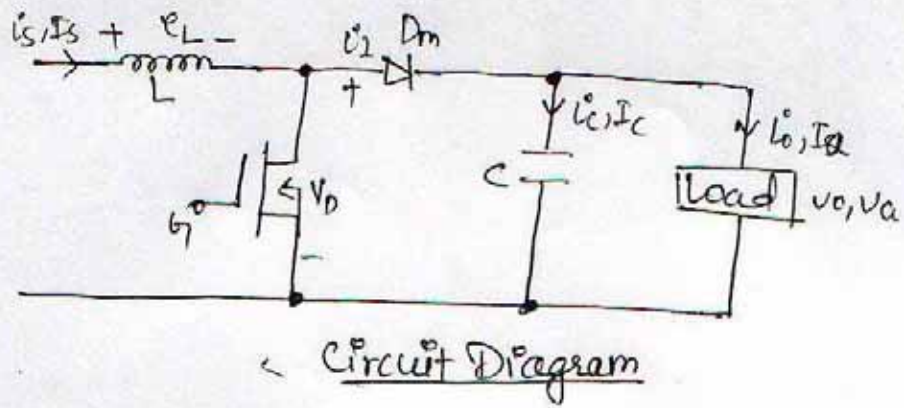


Boost Converter

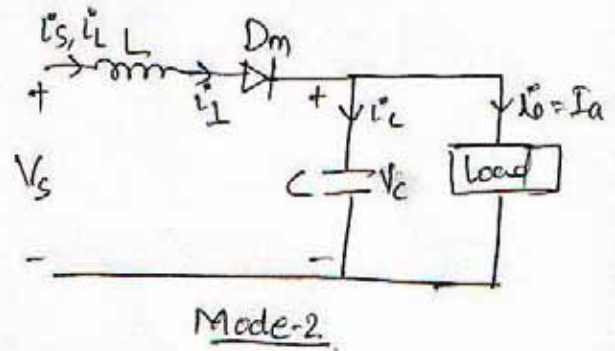

Equivalent Circuits

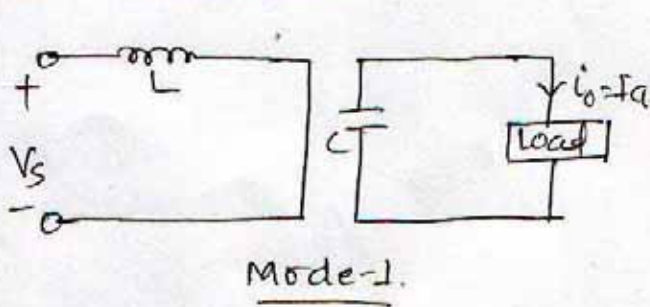

Mode-1

$$V_s = e_L = L \frac{di_L}{dt}$$

$$\text{or, } \int_0^{t_1} V_s dt = \int_{I_1}^{I_2} L di_L$$

$$\text{or, } t_1 \cdot V_s = L(I_2 - I_1)$$

$$\text{or, } t_1 = \frac{L(I_2 - I_1)}{V_s}$$

$$\therefore t_1 = \frac{L \Delta I}{V_s} \quad (1)$$

Mode-2


$$V_s - V_a = e_L = L \frac{di_2}{dt}$$

$$\text{or, } \int_0^{t_2} (V_s - V_a) dt = \int_{I_2}^{I_1} L di_L$$

$$\text{or, } (V_s - V_a) t_2 = L(I_1 - I_2)$$

$$\text{or, } t_2 = \frac{L(I_1 - I_2)}{V_s - V_a} = \frac{L(I_2 - I_1)}{V_a - V_s} = \frac{L \Delta I}{V_a - V_s} \quad (2)$$

Waveforms for Boost Regulator

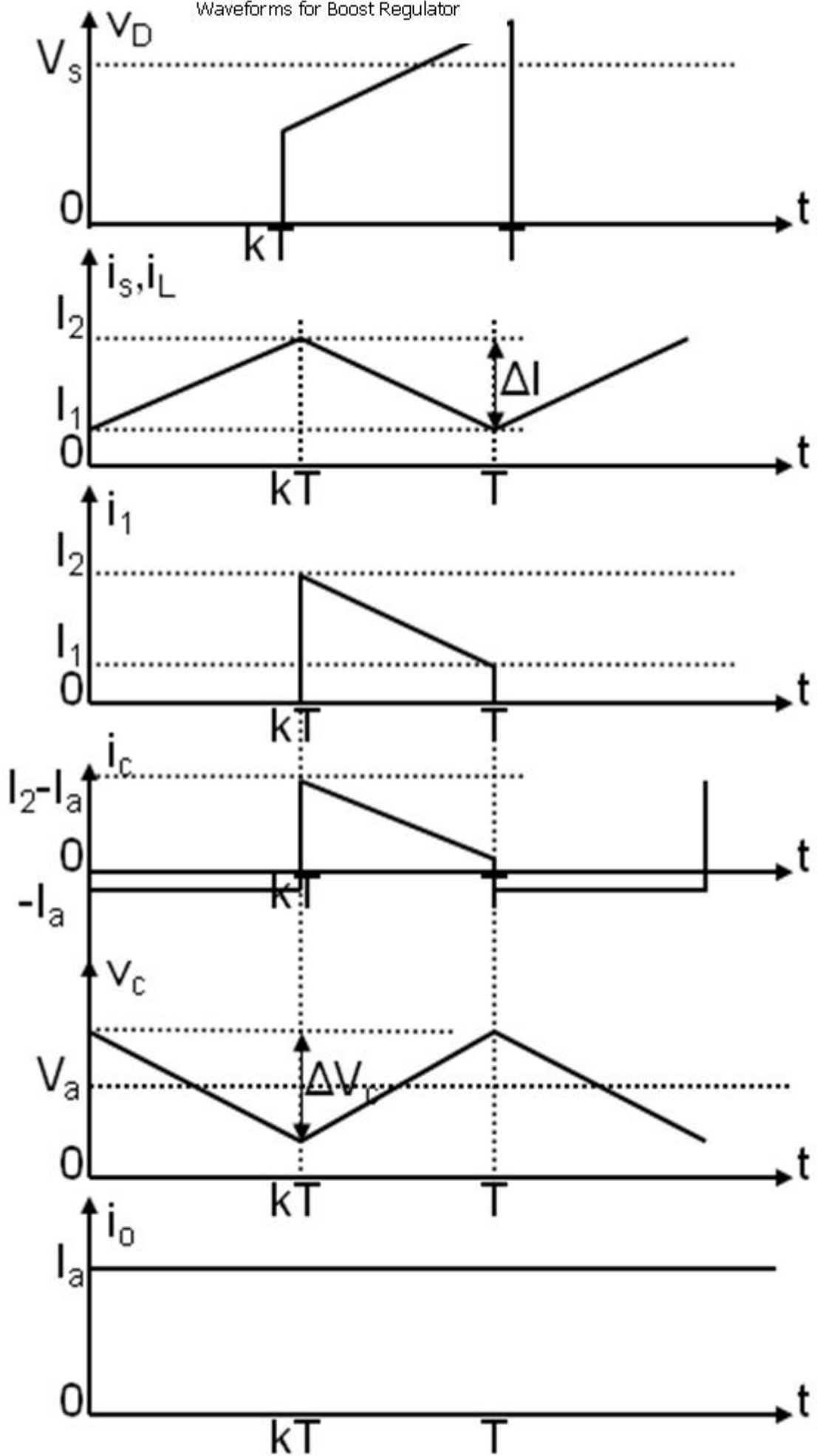

From eqⁿs (i) and (ii),

$$T = t_1 + t_2$$

$$T = \frac{V_a L \Delta I}{V_s (V_a - V_s)} \quad \text{--- (iii)}$$

Further,

$$K = \frac{t_1}{T} = \frac{t_1}{t_1 + t_2} = \frac{(L \Delta I / V_s)}{\frac{L \Delta I}{V_s} + \frac{L \Delta I}{V_a - V_s}} = \frac{1}{1 + \frac{V_s}{V_a - V_s}} = \frac{V_a - V_s}{V_a} = 1 - \frac{V_s}{V_a} \quad \text{--- (iv)}$$

From (iv),

$$1 - K = \frac{V_s}{V_a}$$

$$\therefore \boxed{V_a = \frac{V_s}{1 - K}} \quad \text{for } K < 1, V_a > V_s$$

The transfer function of Boost regulator $\left(\frac{V_a}{V_s}\right) = \frac{1}{1 - K}$

from eqⁿ (iii)

$$\Delta I = \frac{T(V_a - V_s)V_s}{V_a L}$$

$$= \frac{T V_s V_a \left(1 - \frac{V_s}{V_a}\right)}{L V_a}$$

$$= \frac{T V_s [1 - (1 - K)]}{L}$$

$$= \frac{T V_s [K]}{L}$$

$$\boxed{\Delta I = \frac{V_s K}{f L}} \quad \text{--- (v)}$$

When the transistor is on, the capacitor supplies the load current for $t = t_1$. The average capacitor current during time t_1 is $I_c = I_a$ and the peak to peak ripple voltage of capacitor is,

$$\Delta V_c = V_c - V_c \Big|_{t=0}^{t_1} = \frac{1}{C} \int_0^{t_1} I_c dt = \frac{1}{C} \int_0^{t_1} I_a dt = \frac{I_a t_1}{C} \quad \text{--- (vi)}$$

Substituting the value of t_1 from eqⁿ (i),

$$\Delta V_c = \frac{I_a}{C} \left(\frac{L \Delta I}{V_s}\right) = \frac{I_a}{C} \left(\frac{V_a - V_s}{V_a f C}\right) = \frac{I_a V_a \left(1 - \frac{V_s}{V_a}\right)}{V_a f C} = \frac{I_a (K)}{f C} = \frac{I_a K}{f C} \quad \text{--- (vii)}$$

Condition for Continuous Inductor current and Capacitor Voltage.

If I_L is the average inductor current, the inductor ripple current

$$\Delta I = 2I_L$$

$$\text{or, } \frac{V_{SK}}{fL} = 2I_a$$

$$\text{or, } \frac{V_{SK}}{fL} = 2 \cdot \frac{V_a}{R}$$

$$\text{or, } \frac{V_{SK}}{fL} = 2 \cdot \frac{V_s}{(1-K)R}$$

Which gives the critical value of inductor L_c as

$$L_c = L = \frac{K(1-K)R}{2f}$$

If V_c is the average capacitor voltage, the capacitor ripple voltage $\Delta V_c = 2V_a$.

$$\text{or, } \frac{I_a K}{fC} = 2V_a$$

$$\text{or, } \frac{I_a K}{fC} = 2 \frac{V_a}{R}$$

which gives the critical value of capacitor C_c as,

$$C_c = C = \frac{K}{2fR}$$

Numerical

Page 194 (Rashid)