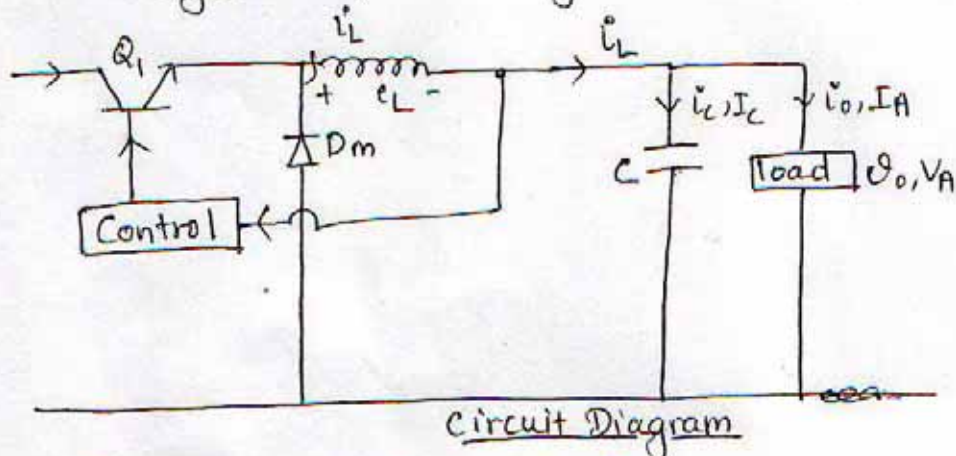


- i) BUCK Converter (regulator)
- ii) Boost " (regulator)
- iii) BUCK-Boost Converter (regulator)

Buck Converter

→ Average output voltage V_a is less than the input voltage V_s .



→ Similar to a step down converter.



Mode-1


- At $t=0$, Q_1 is switched on
- The i_L current which rises flows through L , C and the load.

Mode-2

- At $t=t_1$, Q_1 is switched off
- Freewheeling diode D_m conducts due to energy stored in the inductor. and the inductor current continues to flow through L , C , load and diode D_m .
- The inductor falls until Q_1 is switched on again in the next cycle.

EQUIVALENT CIRCUITS :-

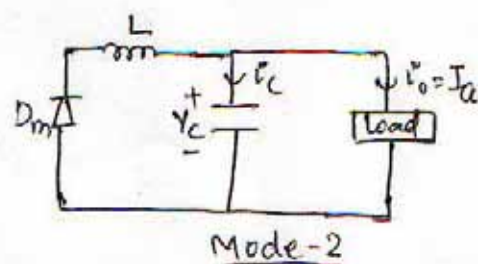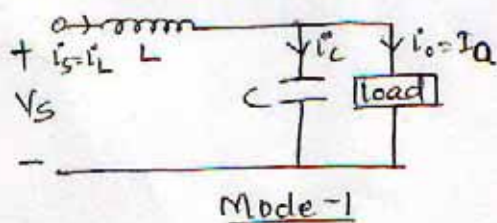

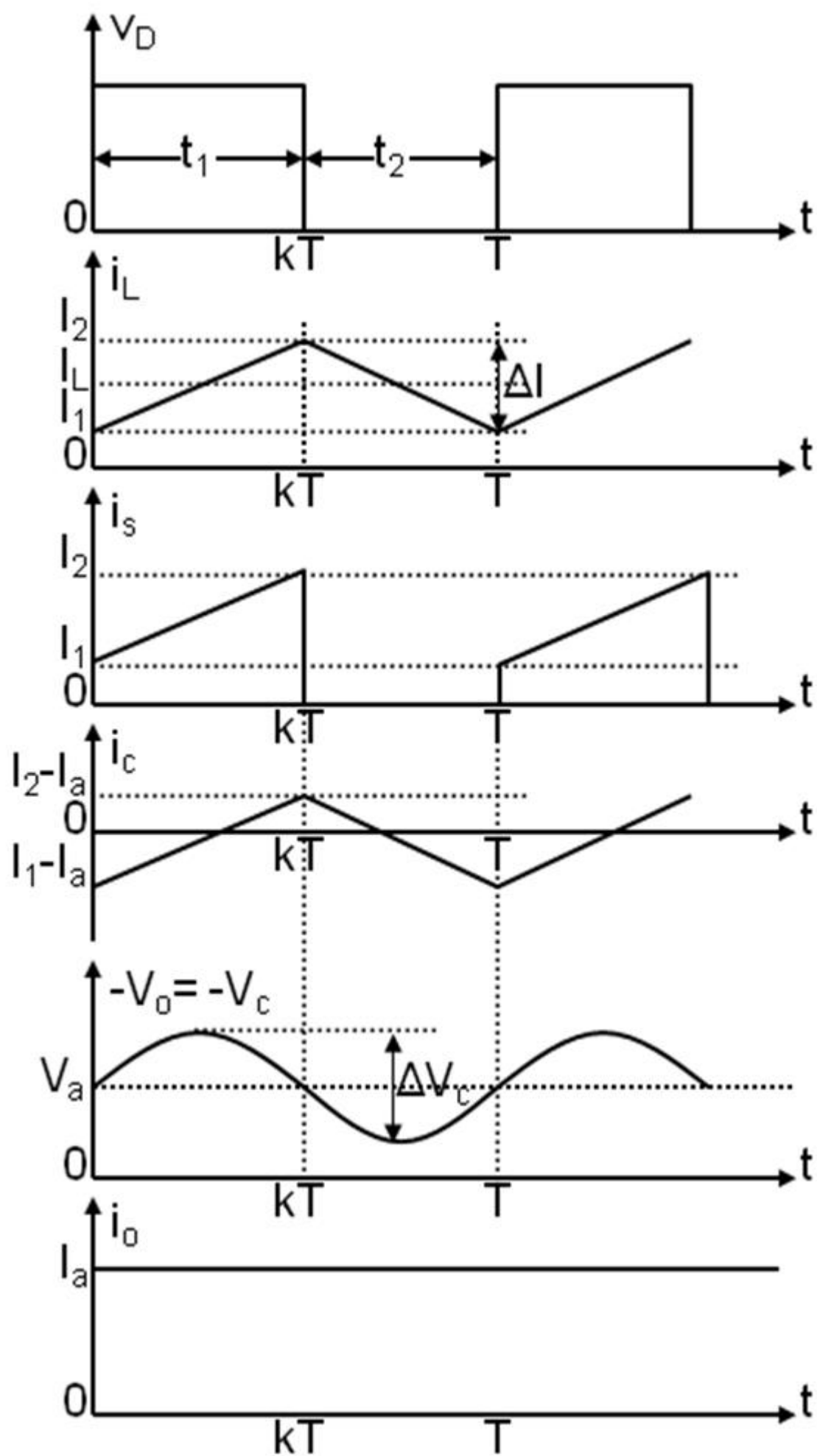

Derivations:-

Mode 1

$$e_L = L \frac{di_L}{dt}, \quad e_L = V_s - V_a \quad \text{--- (i)}$$

$$e_L dt = L di_L$$

$$\int_0^{t_1} e_L dt = \int_{I_1}^{I_2} L di_L$$

$$e_L t_1 = L(I_2 - I_1)$$

$$t_1 = \frac{L(I_2 - I_1)}{e_L} = \frac{L \Delta I}{V_s - V_a} \quad \text{--- (ii)}$$

Mode-2

$$e_L + V_a = 0$$

$$L \frac{di_L}{dt} = -V_a$$

$$L di_L = -V_a dt$$

Integrating,

$$L \int_{I_2}^{I_1} di_L = -V_a \int_0^{t_2} dt$$

$$L(I_1 - I_2) = -V_a t_2$$

$$t_2 = \frac{L(I_1 - I_2)}{-V_a} = \frac{L(I_2 - I_1)}{V_a} \quad \text{--- (iii)}$$

Further,

$$I_2 - I_1 = \Delta I$$

$$\text{so, } t_2 = \frac{L \Delta I}{V_a} \quad \text{--- (iv)}$$

Equating ΔI from eqn (ii) and (iv), we get,

$$\frac{(V_s - V_a)t_1}{L} = \frac{V_a \cdot t_2}{L}$$

$t_1 = kt$ and $t_2 = (1-k)t$ where $k = \text{duty cycle}$

$$\frac{(V_s - V_a)k}{L} = \frac{V_a \cdot (1-k)}{L}$$

$$kV_s - kV_a = V_a - kV_a$$

$$\therefore V_a = kV_s \quad \text{--- (v)}$$

Transfer function of Buck Converter = $\frac{V_o}{V_c} = k$

Assuming a lossless circuit,

$$V_s I_s = V_a I_a = K V_s I_a$$

$$\text{or, } V_s I_s = K V_s I_a$$

$$I_s = K I_a \text{ ————— (VI)}$$

The switching period T can be expressed as,

$$T = \frac{1}{f} = t_1 + t_2$$

$$= \frac{\Delta I L}{V_s - V_a} + \frac{\Delta I L}{V_a} \quad \left[\text{from eq}^n \text{ (V)} \right]$$

$$= \frac{\Delta I L V_s}{V_a (V_s - V_a)}$$

which gives peak to peak ripple current as,

$$\Delta I = \frac{V_a (V_s - V_a) \cdot T}{L V_s}$$

$$= \frac{V_a (V_s - V_a)}{f L V_s}$$

$$= \frac{V_a (V_s - K V_s)}{f L V_s}$$

$$= \frac{K V_s (V_s - K V_s)}{f L V_s}$$

$$= \frac{K V_s - K^2 V_s}{f L}$$

$$= \frac{K V_s (1 - K)}{f L}$$

$$\therefore \Delta I = \frac{V_s K (1 - K)}{f L} \text{ ————— (VII)}$$

Using KCL, $i_L = i_c + i_o$

If we assume load ripple current Δi_o is very small, then $\Delta i_L \approx \Delta i_c$. The average capacitor current which flows into

for $\frac{t_1}{2} + \frac{t_1}{2} = T/2$ will be, $I_c = \frac{\Delta I}{4}$

The capacitor voltage will be,

$$V_c = \frac{1}{C} \int i dt + V_c \Big|_{t=0}$$

and the peak to peak ^{ripple} voltage of the capacitor is,

$$\Delta V_c = V_c - V_c(t=0)$$

$$= \frac{1}{C} \int_0^{T/2} \left(\frac{\Delta I}{4} \right) dt$$

$$= \frac{1}{C} \cdot \frac{\Delta I}{4} \cdot T/2$$

$$\therefore \Delta V_c = \frac{\Delta I}{8 f C}$$

Substituting the value of ΔI , we get,

$$\Delta V_c = \frac{K V_s (1-K)}{8 L C f^2}$$

$$\therefore \Delta V_c = \frac{V_a (1-K)}{8 L C f^2}$$

Condition for Continuous inductor ^{current} and Capacitor Voltage

If I_L is the average inductor current, the inductor ripple current

$$\Delta I = 2 I_L$$

Further, $\Delta I = \frac{V_s K (1-K)}{f L}$

$$2 I_L = \frac{V_s K (1-K)}{f L}$$

$$2 I_a = \frac{V_s K (1-K)}{f L}$$

$$\frac{2 K V_s}{R} = \frac{V_s K (1-K)}{f L}$$

which gives the critical value of inductor L_c as,

$$L_c = L = \frac{(1-K) R}{2 f}$$

If V_c is the average capacitor voltage, the capacitor ripple voltage

$$\Delta V_c = 2 V_a$$

further, $\Delta V_c = \frac{V_a (1-K)}{8 L C f^2}$

$$2 V_a = \frac{V_a (1-K)}{8 L C f^2}$$

which gives critical value of capacitor C_c as

$$C_c = C = \frac{1-K}{16 L f^2}$$