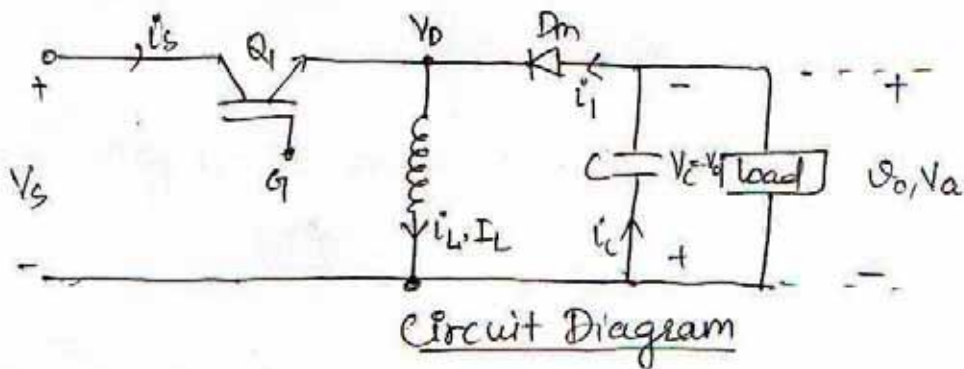




Buck-Boost Converter

→ A Buck-Boost Converter provides an o/p voltage that may be less than or greater than the input voltage.

→ The output voltage polarity, ~~being~~ opposite to that of input voltage so this converter is also known as ~~inverting~~ inverting regulator.



Equivalent Circuits

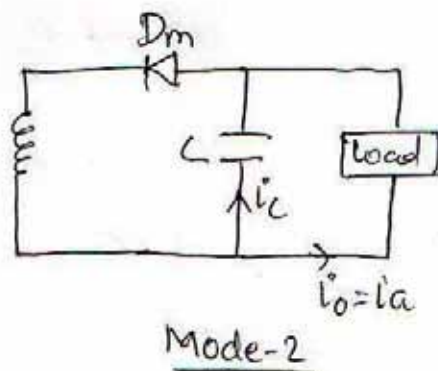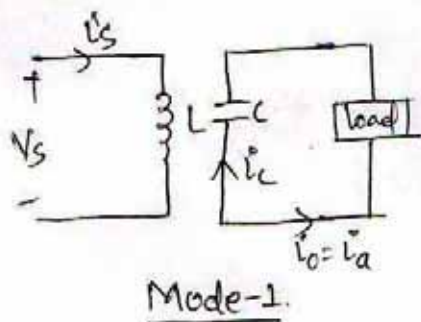

Operation

During mode-1, transistor Q_1 is turned on and diode D_m is reverse biased. The i/p current, which rises linearly (assumed) flows through the inductor L and transistor Q_1 .


During mode-2, transistor Q_1 is switched off and the load current which was flowing through L , would flow through L , C , D_m and the load. The energy stored in inductor L would be transferred to the load and the inductor current would fall until transistor Q_1 is switched on again in the next cycle.

Assuming that the inductor current that rises during time t is linear, we get

$$V_s = L \frac{di_L}{dt} = L \frac{(I_2 - I_1)}{t_1}$$

$$\therefore t_1 = \frac{L \Delta I}{V_s} \quad (1) \quad \text{where, } \Delta I \text{ is the peak to peak ripple current.}$$

Waveforms for Buck Boost Regulator

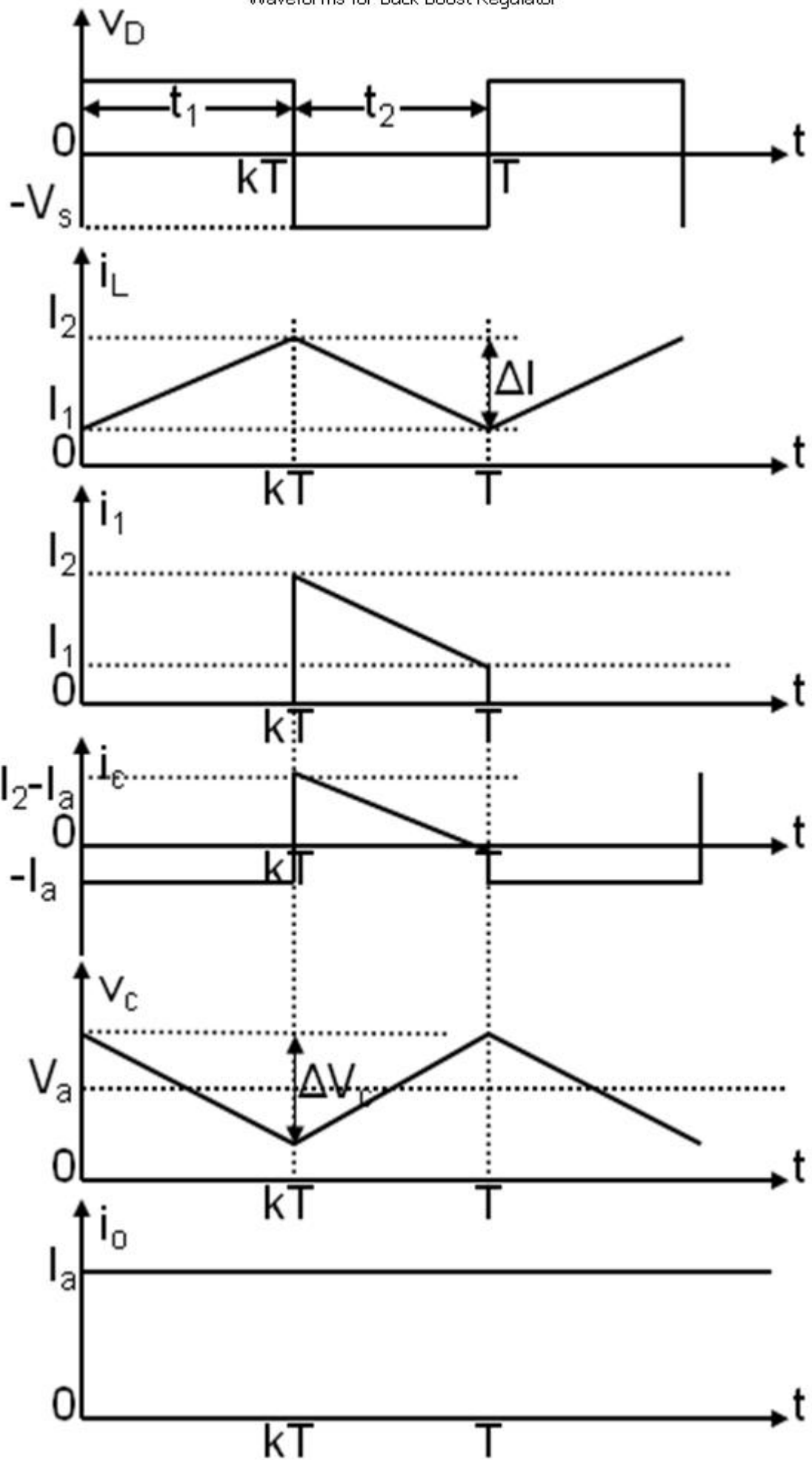

During time t_2 , inductor current falls linearly from I_2 to I_1 .

$$\therefore V_a = -L \frac{\Delta I}{t_2}$$

$$\therefore t_2 = \frac{-L \Delta I}{V_a} \quad \text{--- (2)}$$

From eqⁿ (1) and (2)

$$\Delta I = \frac{t_1 V_s}{L} = -\frac{t_2 V_a}{L} \quad \text{--- (3)}$$

Substituting $t_1 = kT$ and $t_2 = (1-k)T$, we get;

$$\frac{k V_s}{L} = -\frac{(1-k) V_a}{L}$$

$$\text{or, } k V_s = -(1-k) V_a$$

$$\therefore V_a = \frac{-k V_s}{1-k} \quad \text{--- (4)}$$

Further, $t_1 = kT = \left(\frac{-V_a}{V_s - V_a} \right) T = \frac{V_a}{V_a - V_s} \cdot T$

$$\therefore t_1 = \frac{V_a}{f(V_a - V_s)} \quad \text{--- (5) } \left[\because T = \frac{1}{f} \right]$$

For lossless circuit, $V_s I_s = -V_a I_a$

$$\therefore V_s I_s = -\left(\frac{-k V_s}{1-k} \right) I_a$$

$$\text{or, } I_s = \frac{k I_a}{1-k} \quad \text{--- (6)}$$

$$T = t_1 + t_2 = L \Delta I \left(\frac{1}{V_s} - \frac{1}{V_a} \right) = \frac{L \Delta I}{V_s V_a} (V_a - V_s)$$

$$\text{or, } T = \frac{1}{f} = \frac{L \Delta I}{V_s V_a} (V_a - V_s)$$

$$\therefore \Delta I = \frac{V_s V_a}{f L (V_a - V_s)} = \frac{V_s}{f L} \left(\frac{V_a}{V_a - V_s} \right) = \frac{V_s k}{f L} \quad \text{--- (7)}$$

When Q_1 is on, the capacitor supplies the load current for $t = t_1$. The average discharging current of the capacitor is $I_c = I_a$ and the peak to peak ripple voltage of the capacitor is,

$$\Delta V_c = \frac{1}{C} \int_0^{t_1} I_c dt = \frac{1}{C} \int_0^{t_1} I_a dt = \frac{1}{C} I_a t_1 \quad (8)$$

from eqn (5),

$$t_1 = \frac{V_a}{f(V_a - V_s)}$$

$$\therefore \Delta V_c = \frac{1}{C} I_a \cdot \frac{V_a}{f(V_a - V_s)} = \frac{I_a K}{fC} \quad (9)$$

Condition for Continuous Inductor Current and Capacitor Voltage

If I_L is the average inductor current, the inductor ripple current $\Delta I = 2I_L$.

$$\Delta I = 2I_L$$

$$\text{or, } \frac{V_s \cdot K}{fL} = 2I_a$$

~~$$\text{or, } \frac{K V_s}{fL} = 2 \left(\frac{V_a}{R} \right) = 2 \left(\frac{K V_s}{(1-K)R} \right)$$~~

$$\text{or, } \frac{K V_s}{fL} = 2 \left(\frac{V_a}{R} \right) = 2 \left(\frac{K V_s}{(1-K)R} \right) \cdot \frac{1}{R}$$

$$\text{or, } \frac{K V_s}{fL} = \frac{2 K V_s}{(1-K)R}$$

which gives the critical value of inductor L_c as,

$$L_c = L = \frac{(1-K)R}{2f}$$

If V_c is the average capacitor voltage, then, the capacitor ripple voltage $\Delta V_c = 2V_a$.

$$\frac{I_a K}{fC} = 2V_a = 2I_a \cdot R$$

which gives the critical value of capacitor C_c as,

$$C_c = C = \frac{K}{2fR}$$