

Electronic-Circuit II Chap 3 Power Electronics

DC-DC Converters

Instructor:

Ajay Kumar Kadel

Kathmandu Engineering College

Course Homepage


www.courses.esmartdesign.com

DC-DC converters

Electronic Circuit-II

1

DC-DC Conversion

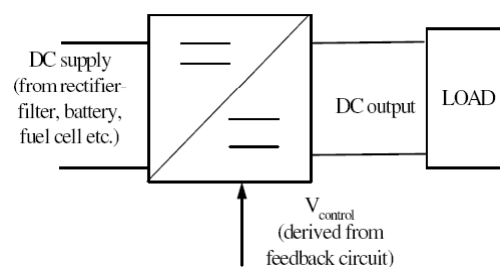

- Choppers: Converts the unregulated DC input to a controlled DC output with a desired voltage level

DC-DC converters

Electronic Circuit-II

2

DC-DC conversion contd

- Earlier, DC-DC converters were called choppers
- In modern power electronics, chopper refers to high power DC-DC converters & SMPS (switching regulators) refers to low power DC-DC converters
- Applications of DC-DC converters:
 - Switched-mode power supply (SMPS), DC motor control, battery chargers

DC-DC converters

Electronic Circuit-II

3

Linear Regulators Review

- Earlier, the linear regulators were the only reliable methods to meet all dc requirements
- Linear Regulator Problems
 - its size and weight
 - Large power dissipation & Low efficiency
 - Limited to low power applications


DC-DC converters

Electronic Circuit-II

4

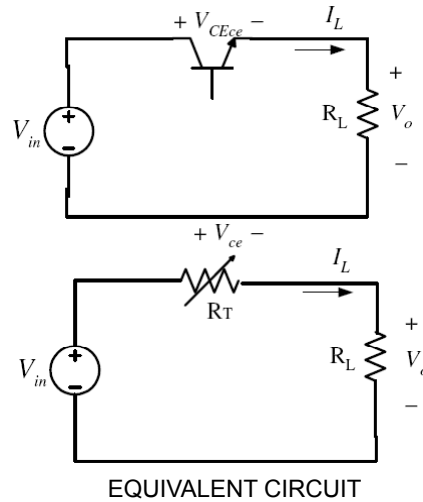Example (Linear Regulator)

- Transistor operated in linear or active region
- Output voltage,
 $V_o = V_{in} - V_{ce}$
- High power loss in BJT
- Low efficiency



DC-DC converters

Electronic Circuit-II

5

Switching Regulators

- Came into existence with the advent of power semiconductor devices
- the semiconductor devices are either **fully switched on** or **fully switched off**
- **Low power consumption** due to lower voltage drop across the semiconductor device
- High Efficiency
- Switched on/off at high frequency so the relative **size** and **weight** of the components needed for its design is comparatively small


DC-DC converters

Electronic Circuit-II


6

Switching Regulators contd..

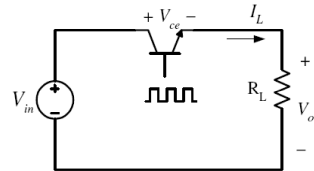- Transistor operated in switched mode
 - Switch closed: Fully on (saturated)
 - Switch opened: Fully off (cut-off)
 - When switch is open, no current flows through it
 - When switch is closed no voltage drop across it
- For an ideal switch power loss is zero since $P=VI$
- Practically, the loss is very small



SWITCHING REGULATOR

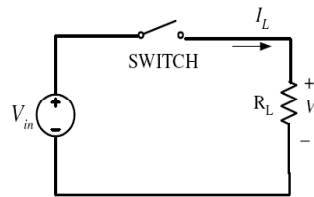

EQUIVALENT CIRCUIT

DC-DC converters

Electronic Circuit-II

7

Switching Regulators contd...

- The high voltage ripple can be controlled by placing a capacitor across the load
- The capacitor is large enough so that its voltage does not have any noticeable change during the time the switch is off
- Circuit can be optimized by placing an inductor in series to limit the current rush
 - Problem:- Since the current in the inductor cannot change suddenly, we have to provide at least one more switch, such as a freewheeling diode, to provide a path for the inductor current when the switch is off (open)

DC-DC converters

Electronic Circuit-II

8

Switching Regulators contd...

- In summary, a good dc-to-dc converter may have, an inductor, a capacitor, a freewheeling diode and an electronic switch.
- The placement of these elements in a circuit dictates the performance of the circuit.
- The three configurations that utilize these circuit elements are:
 - a) **Buck Converter** (lowering the output voltage, step-down application),
 - b) **Boost Converter** (raising the output voltage, step-up application), and
 - c) **Buck-Boost Converter** (lowering or raising the output voltage, step-down or step up application)

DC-DC converters

Electronic Circuit-II

9

Choppers

- DC-DC converters used in high power applications
- Equivalent to transformers in ac
- By switching only a fraction of power is transferred
- Classification
 - Step Down chopper
 - Step Up chopper

DC-DC converters

Electronic Circuit-II

10




Step Down Chopper

Average output vol tage

$$V_a = \frac{1}{T} \int_0^{t_1} v_0 dt = \frac{t_1}{T} V_s = kV_s$$

Average load current

$$I_a = \frac{V_a}{R} = \frac{kV_s}{R}$$

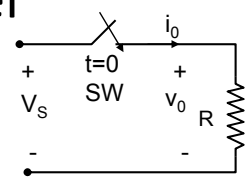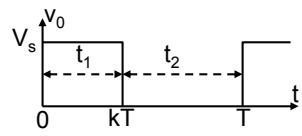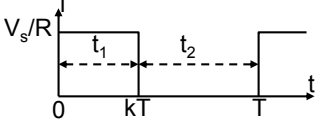T is the chopping period
k is duty cycle of chopper
f is the chopping frequency

DC-DC converters
Electronic Circuit-II
11

Step Down Chopper contd..

rms output voltage




$$V_0 = \left(\frac{1}{T} \int_0^{kT} v_0^2 dt \right)^{1/2} = \sqrt{k} V_s$$

For lossless converter $P_{IN} = P_{OUT}$

$$P_{IN} = \frac{1}{T} \int_0^{kT} v_0 i dt = \frac{1}{T} \int_0^{kT} \frac{v_0^2}{R} dt = k \frac{V_s^2}{R}$$

Effective input resistance seen by source

$$R_i = \frac{V_s}{I_a} = \frac{V_s}{k V_s / R} = \frac{R}{k}$$

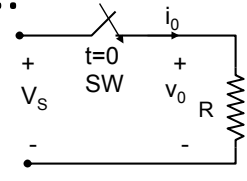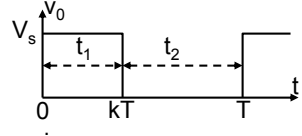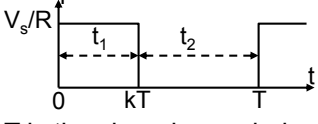T is the chopping period
k is duty cycle of chopper
f is the chopping frequency

DC-DC converters
Electronic Circuit-II
12

Step Down Chopper contd..

For lossy converter

$$P_{IN} = \frac{1}{T} \int_0^{kT} V_s i dt = \frac{1}{T} \int_0^{kT} \frac{V_s (V_s - V_{SW})}{R} dt = k \frac{V_s (V_s - V_{SW})}{R}$$

$$P_{OUT} = \frac{1}{T} \int_0^{kT} \frac{V_0^2}{R} dt = \frac{1}{T} \int_0^{kT} \frac{(V_s - V_{SW})^2}{R} dt = k \frac{(V_s - V_{SW})^2}{R}$$

- Duty cycle can be varied from 0 to 1 by varying t_1 , T or f
- Output voltage V_0 can be varied from 0 to V_s by varying k
- Power flow can be controlled by
 - *Constant frequency operation*: f or T is kept constant and t_1 is varied → *pulse-width modulation*
 - *Variable frequency operation*: t_1 or t_2 is kept constant and f is varied. Operation needs to be carried out over wide range. Generates harmonics and unpredictable frequencies

DC-DC converters



Electronic Circuit-II

13

Step Down Chopper (with RL load)

Operation in 2 modes

- Mode 1 → switch is closed & current flows from supply to load ($0 \rightarrow kT$)
- Mode 2 → switch is open & current continues to flow through free wheeling diode D_M ($kT \rightarrow T$)
- Assume current & voltage rises/falls linearly
 - Actually current rises/falls exponentially with time constant $\tau = L/R$
 - If τ is very large compared to switching period T, linear assumption can be made

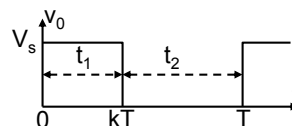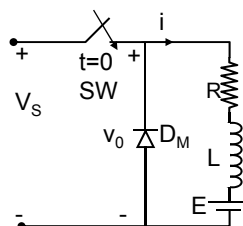

DC-DC converters

Electronic Circuit-II

14

Step Down Converter With RL Load

For mode 1, $0 \leq t \leq t_1 (= kT)$

$$V_s = Ri_1 + L \frac{di_1}{dt} + E$$

Prove \curvearrowright

$$i_1(t) = I_1 e^{-\frac{tR}{L}} + \frac{V_s - E}{R} (1 - e^{-\frac{tR}{L}})$$

At $t = t_1 = kT \Rightarrow i_1(t = t_1) = I_2$

For mode 2, $0 \leq t \leq t_2 (= (1-k)T)$

$$0 = Ri_2 + L \frac{di_2}{dt} + E$$

$$i_2(t) = I_2 e^{-\frac{tR}{L}} + \frac{E}{R} (1 - e^{-\frac{tR}{L}}) \because i_2(t=0) = I_2$$

At $t = t_2 = (1-k)T \Rightarrow i_2(t = t_2) = I_3$

DC-DC convertersElectronic Circuit-II15

Step Down Converter With RL Load

- At the end of mode 2 converter is turned ON again in the next cycle, after time $T = t_1 + t_2$
- Under steady state condition $I_1 = I_3$

$$I_2 = I_1 e^{-\frac{kTR}{L}} + \frac{V_s - E}{R} (1 - e^{-\frac{kTR}{L}})$$

$$I_3 = I_1 = I_2 e^{-\frac{(1-k)TR}{L}} + \frac{E}{R} (1 - e^{-\frac{(1-k)TR}{L}})$$

Solving these two equations

$$I_1 = \frac{V_s}{R} \left(\frac{e^{-\frac{kTR}{L}} - 1}{e^{-\frac{TR}{L}} - 1} \right) - \frac{E}{R}$$

$$I_2 = \frac{V_s}{R} \left(\frac{e^{-\frac{kTR}{L}} - 1}{e^{-\frac{TR}{L}} - 1} \right) - \frac{E}{R}$$

DC-DC convertersElectronic Circuit-II16

Step Down Converter With RL Load

Peak-to-peak current is given by, $\Delta I = I_2 - I_1$

$$\Delta I = \frac{V_s}{R} \frac{1 - e^{-\frac{kTR}{L}} + e^{-\frac{TR}{L}} - e^{-\frac{(1-k)TR}{L}}}{1 - e^{-\frac{TR}{L}}}$$

For maximum ripple,

$$\frac{d(\Delta I)}{dk} = 0$$

$$\frac{V_s}{R \left(1 - e^{-\frac{TR}{L}}\right)} \left(0 + \frac{TR}{L} e^{-\frac{kTR}{L}} + 0 - \frac{TR}{L} e^{-\frac{(1-k)TR}{L}}\right) = 0$$

$$\therefore \frac{TR}{L} e^{-\frac{kTR}{L}} - \frac{TR}{L} e^{-\frac{(1-k)TR}{L}} = 0 \Rightarrow e^{-\frac{kTR}{L}} = e^{-\frac{(1-k)TR}{L}}$$

$$\Rightarrow k = 1 - k \Rightarrow k = \frac{1}{2}$$

DC-DC converters

Electronic Circuit-II

17

Step Down Converter With RL Load

$$\therefore \Delta I_{\max} = \frac{V_s}{R} \frac{1 - e^{-\frac{TR}{2L}} + e^{-\frac{TR}{L}} - e^{-\frac{TR}{2L}}}{1 - e^{-\frac{TR}{L}}} = \frac{V_s}{R} \frac{1 - 2e^{-\frac{R}{2fL}} + e^{-\frac{R}{fL}}}{1 - e^{-\frac{R}{fL}}}$$

$$\Delta I_{\max} = \frac{V_s}{R} \frac{1 - 2e^{-\frac{R}{2fL}} + \left(e^{-\frac{R}{2fL}}\right)^2}{1 - \left(e^{-\frac{R}{2fL}}\right)^2} = \frac{V_s}{R} \frac{\left(1 - e^{-\frac{R}{2fL}}\right)^2}{1 - \left(e^{-\frac{R}{2fL}}\right)^2} = \frac{V_s}{R} \frac{1 - e^{-\frac{R}{2fL}}}{1 + e^{-\frac{R}{2fL}}}$$

$$\Delta I_{\max} = \frac{V_s}{R} \frac{e^{-\frac{R}{4fL}} \left[e^{\frac{R}{4fL}} - e^{-\frac{R}{4fL}} \right]}{e^{-\frac{R}{4fL}} \left[e^{\frac{R}{4fL}} + e^{-\frac{R}{4fL}} \right]} = \frac{V_s}{R} \frac{\sinh\left(\frac{R}{4fL}\right)}{\cosh\left(\frac{R}{4fL}\right)} = \frac{V_s}{R} \tanh\left(\frac{R}{4fL}\right)$$

$$\text{for } 4fL \gg R \Rightarrow \tanh \theta \approx \theta \Rightarrow \Delta I_{\max} = \frac{V_s}{4fL}$$

DC-DC converters

Electronic Circuit-II

18

Step Down Converter With RL Load

- For discontinuous current flow
- low frequency, low output current & large off-time
- Current continuous if $L/R \gg T$ or $Lf \gg T$
- For discontinuous current $i_1=0$

$$i_1(t) = \frac{V_s - E}{R} \left(1 - e^{-\frac{tR}{L}}\right) \text{ but at } t = kT, i_1(t) = I_2$$

$$I_2 = \frac{V_s - E}{R} \left(1 - e^{-\frac{kTR}{L}}\right)$$

$$i_2(t) = I_2 e^{-\frac{tR}{L}} + \frac{E}{R} \left(1 - e^{-\frac{tR}{L}}\right) \text{ for } 0 \leq t \leq t_2$$

$$i_2(t = t_2) = I_3 = I_1 = 0$$

$$\Rightarrow t_2 = \frac{L}{R} \ln\left(1 + \frac{RI_2}{E}\right) = \frac{L}{R} \ln\left(1 + \frac{V_s - E}{E} \left(1 - e^{-\frac{kTR}{L}}\right)\right)$$

DC-DC converters

19

Step Up Converter

- Switch closed for time t_1
 - Inductor current rises and energy is stored
 - Switch open for time t_2
 - Energy transferred to load through diode
- Voltage across the inductor when ON is

$$V_L = L \frac{di}{dt}$$

Peak – to – peak current in the inductor is




$$\Delta I = \frac{V_s}{L} t_1$$

Average output voltage

$$V_0 = V_s + L \frac{\Delta I}{t_2} = V_s \left(1 + \frac{t_1}{t_2}\right) = V_s \frac{1}{1 - k}$$

DC-DC converters

Electronic Circuit-II

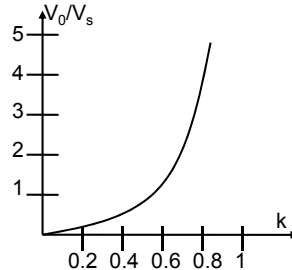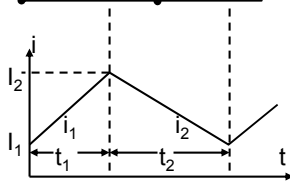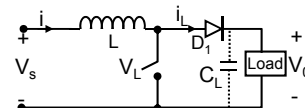

20

Step Up Converter

- Capacitor connected output is averaged
- Voltage can be varied by varying k
- As k increases sensitivity decreases
- Converter cannot work continuously for k=1
- Can be used to transfer voltage from one source to another




When switch is closed (mode 1)

$$V_s = L \frac{di_1}{dt}$$

$$i_1(t) = \frac{V_s}{L} t + I_1 \quad I_1 \equiv \text{Initial current for mode 1}$$

The current must rise,
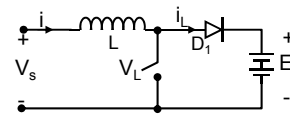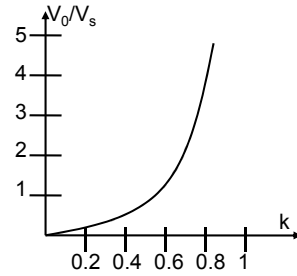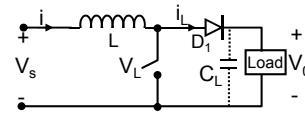
$$\therefore \frac{di_1}{dt} > 0 \text{ or } V_s > 0$$



DC-DC converters

Electronic Circuit-II

21

Step Up Converter

When switch is open (mode 2)



$$V_s = L \frac{di_2}{dt} + E$$

$$i_2(t) = \frac{V_s - E}{L} t + I_2 \quad I_2 \equiv \text{Initial current for mode 2}$$

The current must fall for stable operation,

$$\therefore \frac{di_2}{dt} < 0 \text{ or } V_s < E$$

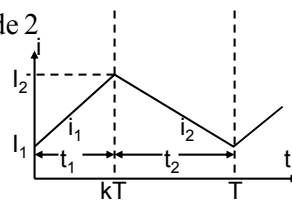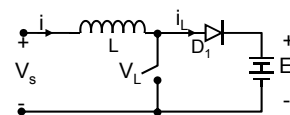- For controllable power transfer $0 < V_s < E$



DC-DC converters

Electronic Circuit-II

22

Step Up Converter With Resistive Load

When switch is closed (mode 1)

$$V_s = L \frac{di_1}{dt}$$

$$i_1(t) = \frac{V_s}{L} t + I_1 \text{ for } 0 \leq t \leq kT$$



$$I_2 = i_1(t = kT) = \frac{V_s}{L} kT + I_1$$

When switch is open (mode 2)

$$V_s = Ri_2 + L \frac{di_2}{dt} + E$$

$$i_2(t) = \frac{V_s - E}{L} \left(1 - e^{-\frac{tR}{L}} \right) + I_2 e^{-\frac{tR}{L}} \text{ for } 0 \leq t \leq (1-k)T$$

$$I_1 = i_2(t = (1-k)T) = \frac{V_s - E}{L} \left(1 - e^{-\frac{(1-k)TR}{L}} \right) + I_2 e^{-\frac{(1-k)TR}{L}}$$

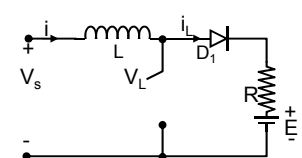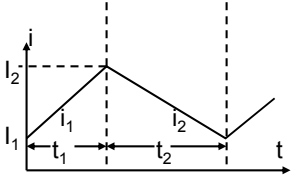DC-DC converters
Electronic Circuit-II
23

Step Up Converter With Resistive Load



By solving the equations

$$I_1 = \frac{V_s kT}{L} \frac{e^{-\frac{(1-k)TR}{L}}}{1 - e^{-\frac{(1-k)TR}{L}}} + \frac{V_s - E}{R}$$

$$I_2 = \frac{V_s kT}{L} \frac{1}{1 - e^{-\frac{(1-k)TR}{L}}} + \frac{V_s - E}{R}$$

The ripple current is given by


$$\Delta I = I_2 - I_1 = \frac{V_s kT}{L}$$

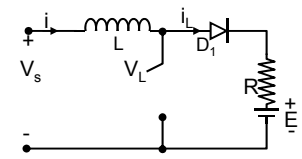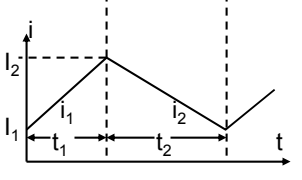
DC-DC converters
Electronic Circuit-II
24

Chopper Classification

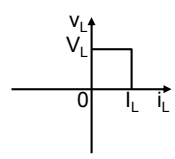
- On the basis of power flow, i.e. on the basis of current and voltage flows choppers can be divided into
 - First quadrant converter (Class A)
 - Second quadrant converter (Class B)
 - First & second quadrant converter (Class C)
 - Third & fourth quadrant converter (Class D)
 - Four-quadrant converter (Class E)




First

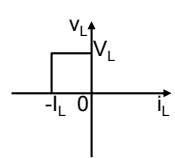


Second

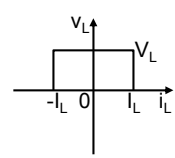


First & Second

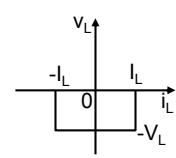

Third & Fourth

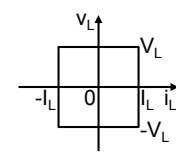

Four-quadrant

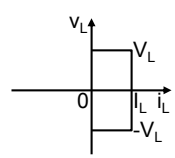

Class D

DC-DC converters
Electronic Circuit-II
25




Chopper Classification contd..

First Quadrant Converter

- Current flows into the load
- Voltage & current positive
- Single Quadrant converter
- Acts as a rectifier

Second Quadrant Converter

- Current flows out of the load
- Load voltage positive
- Load Current Negative
- Single Quadrant converter
- Acts as an inverter
- Battery E is part of the load

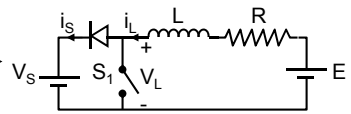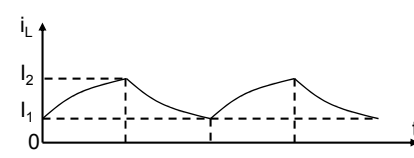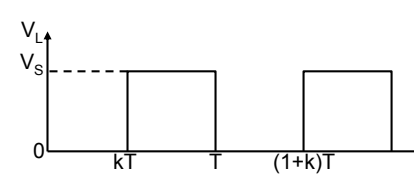DC-DC converters
Electronic Circuit-II
26




Chopper Classification

Second Quadrant Converter Operation

- When switch S_1 is ON voltage E drives current through inductor
- Voltage V_L becomes zero

$$0 = L \frac{di_L}{dt} + Ri_L + E$$

$$i_L = I_1 e^{-\frac{R}{L}t} - \frac{E}{R} \left(1 - e^{-\frac{R}{L}t} \right) \text{ for } 0 \leq t \leq kT$$
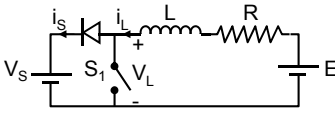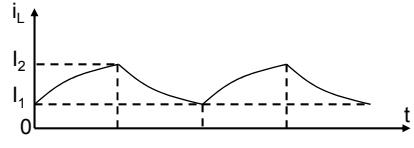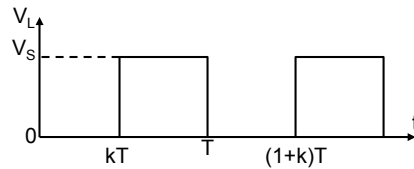
$$i_L(t=0) = I_1 \quad i_L(t=kT) = I_2$$




DC-DC converters Electronic Circuit-II 27

Chopper Classification

Second Quadrant Converter Operation

- When switch S_1 is OFF energy stored in inductor is returned to supply V_s via diode D
- Current i_L falls




$$V_s = L \frac{di_L}{dt} + Ri_L + E$$

$$i_L = I_2 e^{-\frac{R}{L}t} - \frac{V_s - E}{R} \left(1 - e^{-\frac{R}{L}t} \right) \text{ for } kT \leq t \leq T$$

$$i_L(t=kT) = I_2$$



Steady-state

$$i_L(t=T) = I_1 \text{ continuous current}$$
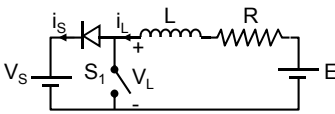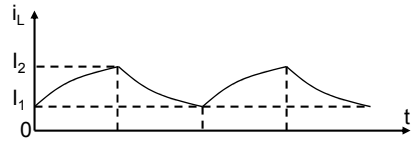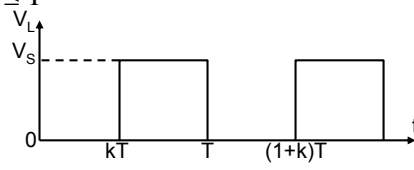
$$i_L(t=T) = 0 \text{ dis-continuous current}$$




DC-DC converters Electronic Circuit-II 28

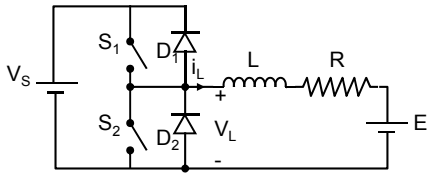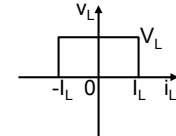Chopper Classification



First & Second

First & Second Quadrant Converter

- Load current is either positive or negative
- Load voltage is always positive
- S_1 & D_2 operate as first quadrant converter
- S_2 & D_1 operate as second quadrant converter
- Firing of both switches must not occur together → to prevent short-circuit
- Can operate as a rectifier or inverter

DC-DC converters
Electronic Circuit-II
29

Chopper Classification

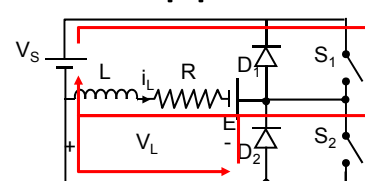
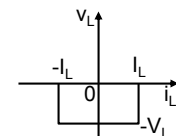
Third & Fourth

Third & Fourth Quadrant Converter

- Load current is either positive or negative
- Load voltage is always negative
- S_1 & D_2 operate to yield both negative voltage and load current
- When S_1 is closed a negative current flows through the load
- When S_1 is open current free wheels through diode D_2

DC-DC converters
Electronic Circuit-II
30

Chopper Classification

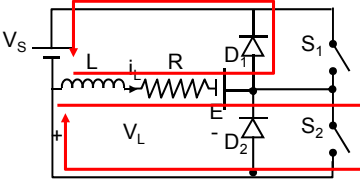
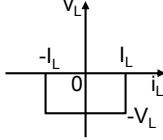
Third & Fourth

Third & Fourth Quadrant Converter

- S_2 & D_1 operate to yield negative voltage and positive load current
- When S_2 is closed a positive current flows through the load
- When S_2 is open current free wheels through diode D_1
- This is a negative two-quadrant converter
- Can operate as a rectifier or inverter

DC-DC converters
Electronic Circuit-II
31

Chopper Classification

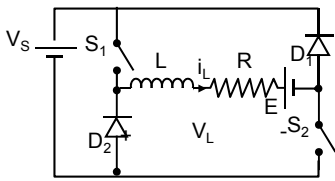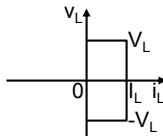Class D

Class D Converter

- The load voltage is always positive
- The load current is either positive or negative
- S_1 & S_2 operate to yield positive voltage and load current
- D_1 & D_2 operate to yield positive load current and negative voltage
- Can operate as a rectifier or inverter

DC-DC converters
Electronic Circuit-II
32

Chopper Classification

S_4 (modulating), D_2	S_1 (modulating), S_2 (continuously ON)
D_1, D_2	S_2, D_4
S_3 (modulating), S_4 (continuously ON)	S_2 (modulating), D_4
S_4, D_2	D_3, D_4

Four-Quadrant Converter

- Load current is either positive or negative
- Load voltage is either positive or negative
- One first & second quadrant converter and one third & fourth quadrant converter joined to form four-quadrant converter

Inverting $V_L +ve$ $I_L -ve$	Rectifying $V_L +ve$ $I_L +ve$
Rectifying $V_L -ve$ $I_L -ve$	Inverting $V_L -ve$ $I_L +ve$

DC-DC converters
Electronic Circuit-II
33