

4.0 COMMUNICATION SYSTEMS (Amp. Modulation & Demodulation circuits)

Prepared By:- Ajay Kumar Kadel, Kathmandu Engg. College

1. Amplitude Modulator in the amplifier circuit

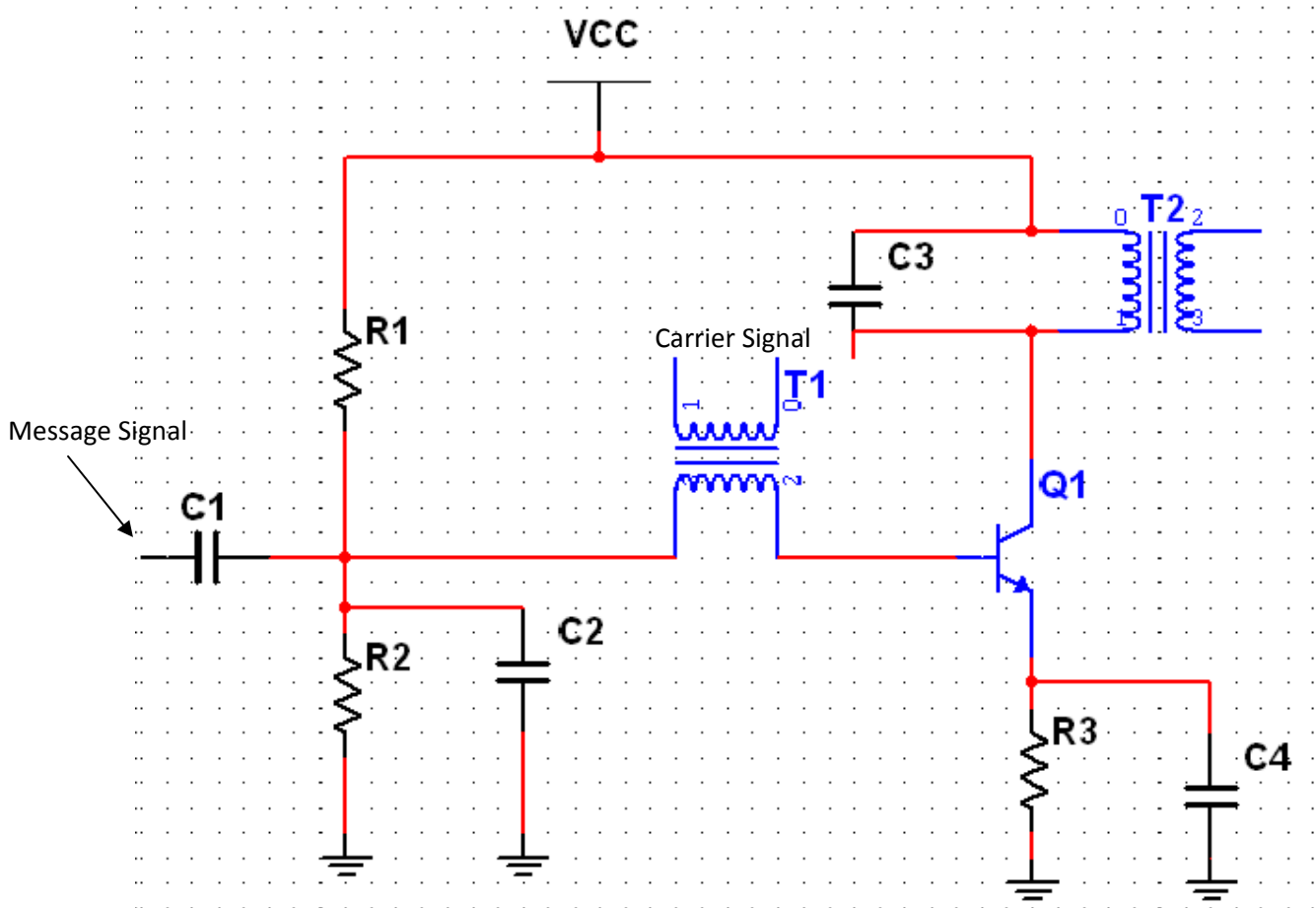


Fig. 1 Amplitude Modulated transistor amplifier with base injection

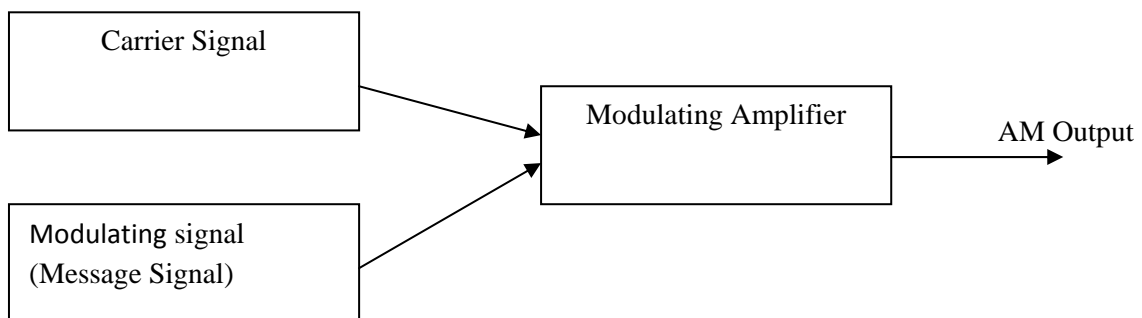


Fig 2. Block Diagram of Amplitude Modulation in the Amplifier Circuit

- The above fig. shows amplitude modulated transistor amplifier with base injection in the common emitter configuration.

- The transistor is powered by V_{cc} through the voltage divider network. The carrier signal is coupled to the base of the transistor by transformer T1 and modulating signal is coupled through C_1 .
- The modulating signal causes the bias to increase and decrease.
- The transformer T_2 couples the modulated signal to the load of the amplifier.

2. Amplitude Modulator in the Oscillator circuit

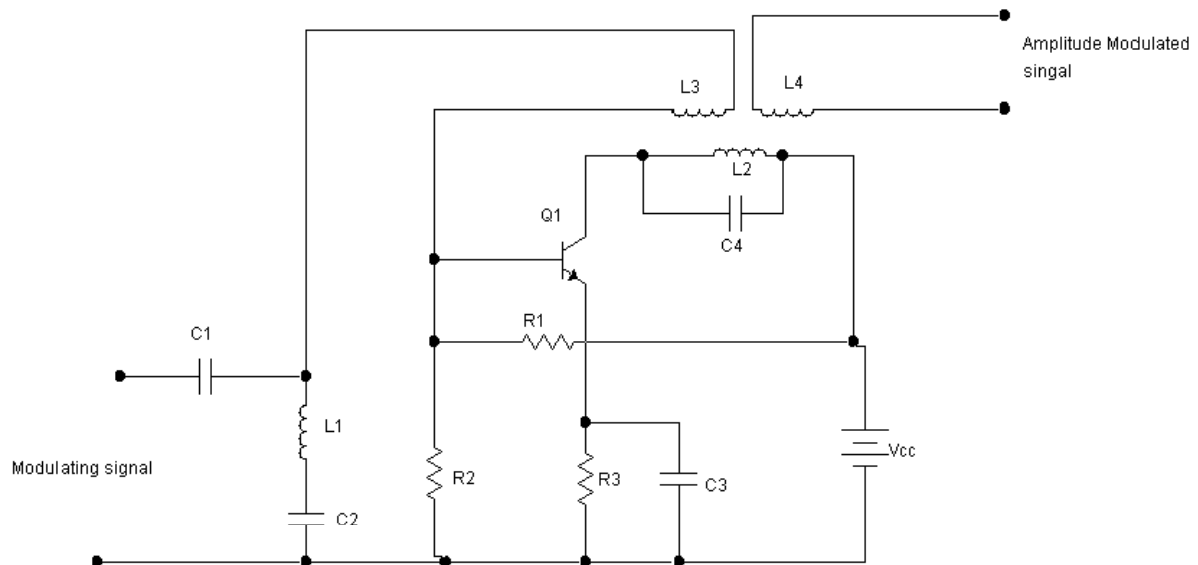


Fig. 3 Amplitude Modulated transistor Oscillator with base injection

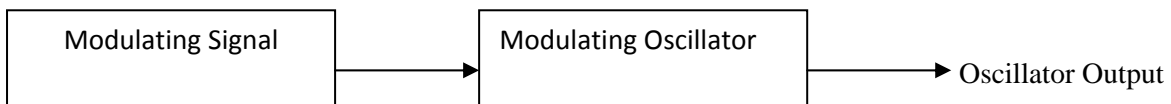


Fig. 4 Block Diagram of Amplitude Modulation in the Oscillator Circuit

- Carrier wave is generated by an LC tank circuit of the oscillator. (i.e. the combination of L_2 and C_4)
- Modulating signal is directly fed in along with the fed-back carrier wave
- The transistor in CE configuration
- Secondary winding L_3 provides positive feedback for transistor Q_1
- Secondary winding L_4 couples the modulated output to oscillator load
- R_1 & R_2 provides biasing for the transistor
- L_1 & C_2 are made resonant to carrier frequency thereby providing low impedance path
- The impedance of L_1 & C_2 for relatively low frequency modulating signal is very high. This has negligible loading effect to the modulating source
- Fixed bias R_1 & R_2 , supply, the feedback voltage from L_3 and the modulating signal voltage varies the bias increasing the gain thereby increasing the amplitude of the carrier signal (couples to output)