

Electronic-Circuit II

Chap 3 Power Electronics

Silicon Controlled Rectifier

Instructor:

Ajay Kumar Kadel
Kathmandu Engineering College

Course Homepage

www.courses.esmartdesign.com

Introduction

- Thyristor Family
 - SCR
 - Triac
 - GTO
 - MCT
 - IGCT
- Thyristors have been the traditional workhorses for bulk power conversion and control in industry
- The term “thyristor” came from its gas tube equivalent, thyatron

Silicon Controlled Rectifier (SCR)

- Belongs to a thyristor family of semiconductors
- The **Silicon Controlled Rectifier** is the most popular of the thyristor family of four layer regenerative devices so it is used synonymously with thyristor
- Compared to transistors
 - Have lower on-state conduction losses & handle higher power
 - Have slower switching speeds and higher switching losses


Silicon Controlled Rectifier

Electronic Circuit-II

3

SCR Introduction

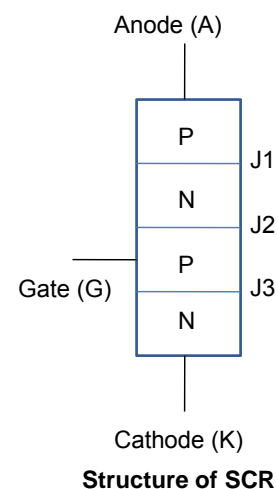- A thyristor is a four layered semiconductor device of p-n-p-n structure with three p-n junction
- It has 3 p-n junctions and 3 terminals
- It is normally turned on by the application of a gate pulse when a forward bias voltage is present at the main terminals.
- However, being regenerative or 'latching', it cannot be turned off via the gate terminals




Silicon Controlled Rectifier

Electronic Circuit-II

4

SCR Characteristics

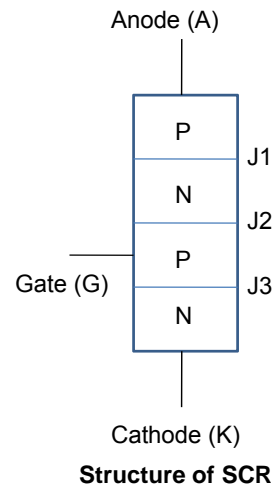- When V_{AK} = positive (anode made more positive)
 - Junction J_1 and J_3 are forward biased
 - Junction J_2 is reverse biased
 - Small leakage current flows from anode to cathode (I_D = off-state current)
 - Forward blocking or off-state condition




Silicon Controlled Rectifier

Electronic Circuit-II

5

SCR Characteristics contd...

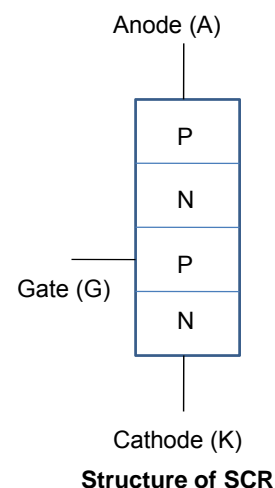- When V_{AK} is increased sufficiently
 - Such that J_2 breaks down (avalanche)
 - $V_{AK} = V_{BO}$ (forward breakdown voltage)
 - Large forward current (Device ON)
 - Typical voltage drop = 1V (Ohmic drop)
 - Anode current limited by external resistance
 - Anode current must exceed latching current
 - Works as a normal diode once turned ON



Silicon Controlled Rectifier



Electronic Circuit-II

6

SCR Characteristics contd..

- When V_{AK} = negative

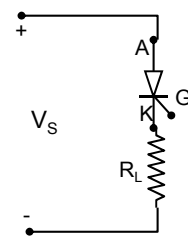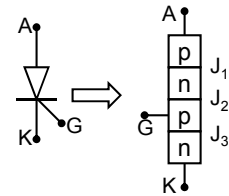- Junction J1 and J3 are reverse biased
- Junction J2 is forward biased
- Small leakage current flows from cathode to anode (IR= reverse current)
- Reverse blocking state



Silicon Controlled Rectifier

Electronic Circuit-II

7


SCR Characteristics contd..

- When V_{AK} is greater than or equal to V_{BO}

- Device turned ON
- Anode current $> I_L$ in order to maintain the amount of carrier flow across the junction
- Otherwise the device reverts back to off-state

- Latching Current

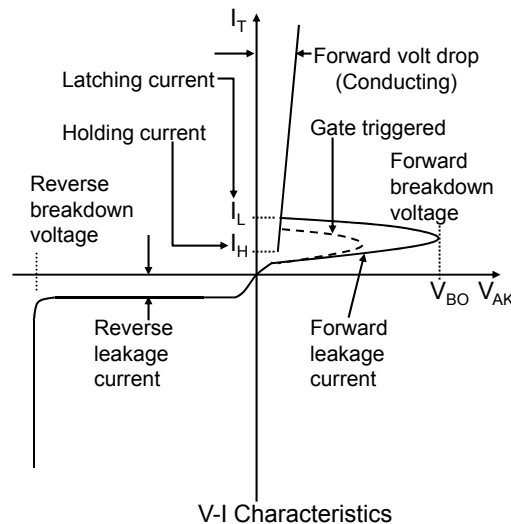- Minimum anode current to maintain the thyristor in on-state immediately after it has been turned ON and gating signal has been removed




Silicon Controlled Rectifier

Electronic Circuit-II

SCR Characteristics contd..

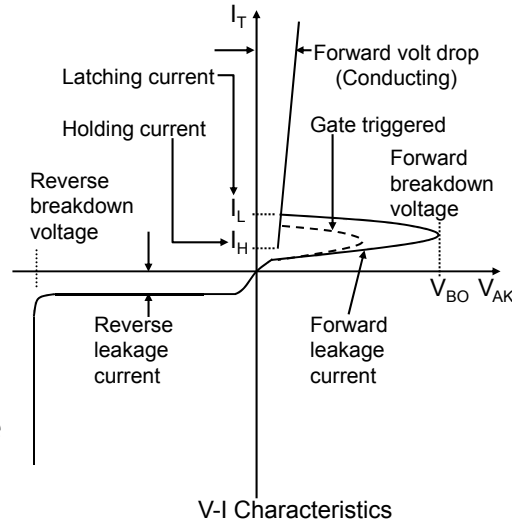- Once the device is ON it operates a normal diode and there is no control over the device
- The device conducts as if there is an absence of the depletion region
- In ON state if the anode current is lowered below the Holding current, depletion region forms due to reduced no. of carriers and switches to blocking state




ElectroniB Circuit-II

Silicon Controlled Rectifier

SCR Characteristics contd..

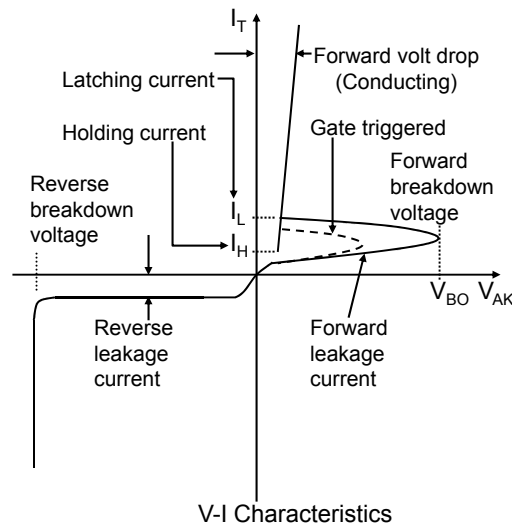- **Holding Current**
 - Minimum anode current to maintain the thyristor in ON state
- Switching thyristor by making $V_{AK} > V_{BO}$ leads to destructive turn ON
- Thyristor can be turned ON with $V_{AK} < V_{BO}$ and applying positive gate voltage
- Once conducting the gate signal can be removed if the anode current > holding current




ElectroniB Circuit-II

Silicon Controlled Rectifier

Two Transistor model of thyristor

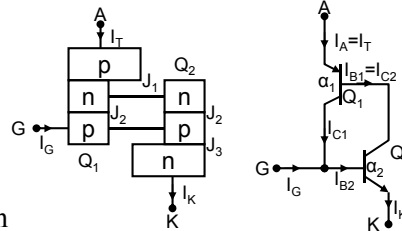- Can be separated into pnp (Q1) & npn (Q2)



$$I_C = \alpha I_E + I_{CBO}$$

$$\alpha \approx \frac{I_C}{I_E} = \text{common base current gain}$$

$$I_{C1} = \alpha_1 I_A + I_{CBO1}$$

$$I_{C2} = \alpha_2 I_K + I_{CBO2}$$

$$I_A = I_{C1} + I_{C2} = \alpha_1 I_A + I_{CBO1} + \alpha_2 I_K + I_{CBO2}$$

$$\text{For a gating current } I_G, I_K = I_A + I_G$$

$$I_A = \frac{I_{CBO1} + I_{CBO2} + \alpha_2 I_G}{1 - (\alpha_1 + \alpha_2)}$$

Electronic Circuit-II

11

Silicon Controlled Rectifier

Two transistor model contd...

$$I_A = \frac{I_{CBO1} + I_{CBO2} + \alpha_2 I_G}{1 - (\alpha_1 + \alpha_2)}$$


- The device is in off state when $\alpha_1 + \alpha_2 \ll 1$. This happens for lower value of I_E (or I_A, I_K). In this case I_A is equal to the sum of the leakage currents.
- When $\alpha_1 + \alpha_2$ is nearly equal to 1, the current increases without limit and the device is in the ON state

Silicon Controlled Rectifier

Electronic Circuit-II

12

Regenerative Feedback in SCR

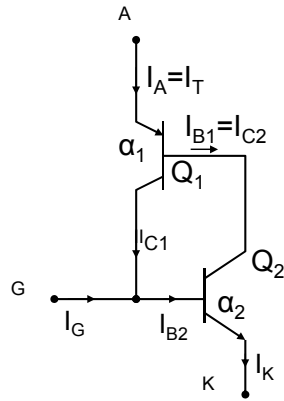

- If I_{C1} increases, I_{B2} increases which increases I_{C2} ($I_{C2} = \beta I_{B2}$). This increases I_{B1} ($I_{B1} = I_{C2}$) which then further increases I_{C1} ($I_{C1} = \beta I_{B1}$)
- $I_{C1} \uparrow \rightarrow I_{B2} \uparrow \rightarrow I_{C2} \uparrow \rightarrow I_{B1} \uparrow \rightarrow I_{C1} \uparrow$

Silicon Controlled Rectifier


Electronic Circuit-II

13

Two-transistor transient model

$$\dot{i}_{j2} = \frac{d(q_{j2})}{dt} = \frac{d(C_{j2}V_{j2})}{dt}$$
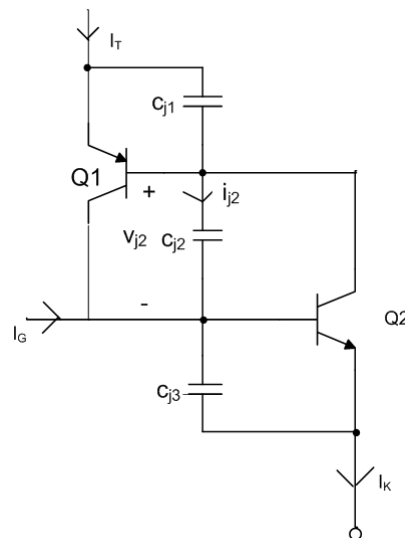
$$\dot{i}_{j2} = V_{j2} \frac{d(C_{j2})}{dt} + C_{j2} \frac{d(V_{j2})}{dt}$$



Silicon Controlled Rectifier

Electronic Circuit-II

14

Numerical

- The capacitance of reverse-biased junction J2 in a thyristor is $C_{J2} = 20 \text{ pF}$ and can be assumed to be independent of the off-state voltage. The limiting value of the charging current to turn on the thyristor is 16 mA. Determine the critical value of dv/dt .


(Ans: $800\text{V}/\mu\text{s}$)

Methods to turn on the SCR

- Thermal
 - High temperature \rightarrow increase in electron-hole pairs \rightarrow increase in leakage current \rightarrow increase in α_1 and α_2
 - Regenerative action leads to $(\alpha_1 + \alpha_2) = \text{unity}$ turning ON the device
 - Thermal runaway must be avoided
- Light
 - Light striking the junction may increase electron hole pairs
- High Voltage
 - When $V_{AK} > V_{BO}$
 - Maybe destructive TURN ON

Thyristor Turn on Methods contd.

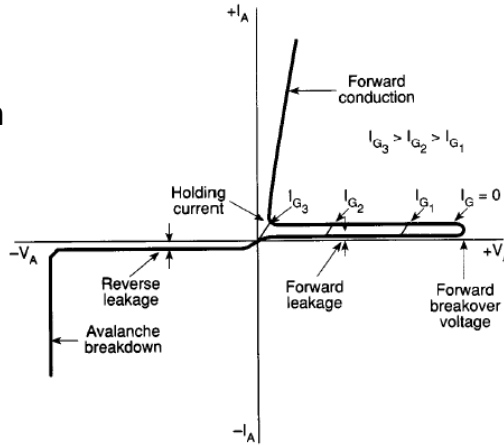- When the thyristor is forward biased
 - Injection of gate current → applying +ve voltage between gate and cathode
 - Increasing gate current → increases gating voltage → reduces forward blocking voltage
- Gating signal should be removed after turn ON to decrease power loss




Silicon Controlled Rectifier

Electronic Circuit-II

17

Thyristor turn on Parameters.....

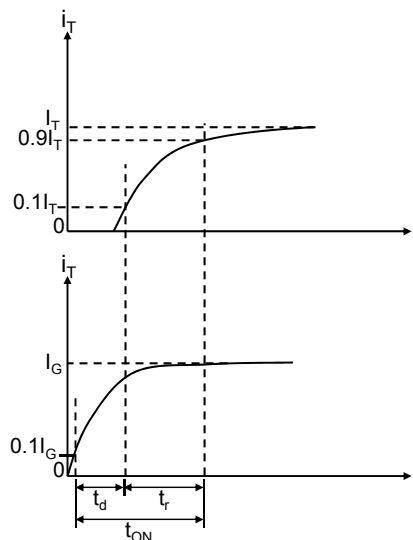- Device turns ON after time delay t_{ON}
- t_{ON} = delay time (t_d) + rise time (t_r)
- t_{ON} → time interval between 10% gate current to 90% steady state current
- t_d → time interval between 10% gate current to 10% ON state current
- t_r → time interval between 10% ON current to 90% ON state current



Silicon Controlled Rectifier

Electronic Circuit-II

18

Assignment-1

- Write short notes on Thyristor Commutation Techniques, DIAC and TRIAC
 - Deadline: Tomorrow 2:00 PM


Silicon Controlled Rectifier

Electronic Circuit-II

19

SCR Half Wave Rectifier

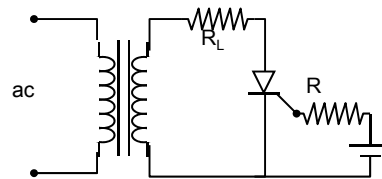- Same as a normal diode rectifier
- The average output voltage however differs
- Conduction is defined by the phase of gating signal



If $v = V_m \sin \theta$ is the input signal

Average output is,

$$V_{av} = \frac{1}{2\pi} \int_{\alpha}^{\pi} V_m \sin \theta d\theta = \frac{V_m}{2\pi} [-\cos \theta]_{\alpha}^{\pi}$$

$$V_{av} = \frac{V_m}{2\pi} (1 + \cos \alpha)$$


Silicon Controlled Rectifier

Electronic Circuit-II

20

SCR Full wave Rectifier

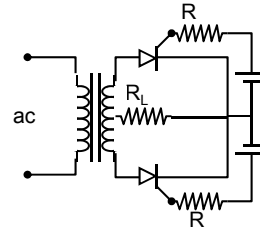- Same a normal diode rectifier
- The average output voltage however differs
- Conduction is defined by the phase of gating signal




If $v = V_m \sin \theta$ is the input signal

Average output is,

$$V_{av} = \frac{2}{2\pi} \int_{\alpha}^{\pi} V_m \sin \theta d\theta = \frac{V_m}{\pi} [-\cos \theta]_{\alpha}^{\pi}$$
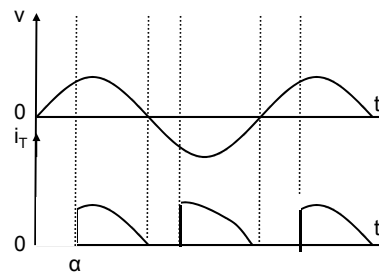
$$V_{av} = \frac{V_m}{\pi} (1 + \cos \alpha)$$



Silicon Controlled Rectifier

Electronic Circuit-II

21