

# CHAPTER 6

## OSCILLATORS

Course Instructor (2EA)

**AJAY KUMAR KADEL**

**ASSISTANT LECTURER (KEC, Kalimati)**

Course Homepage:

[www.courses.esmartdesign.com](http://www.courses.esmartdesign.com)

**JAN 2009**

1

## CHAPTER OUTLINE

- A.C .Signal Sources
- Oscillators Introduction
- Difference between amplifier and oscillators
- Frequency Stability of Oscillator
- Principle Of Oscillator
- Barkhausen Criterion
- RC Oscillators
- LC Oscillators
- Astable Multivibrators
- **Square Wave Generators**
- **Triangular Wave generators**
- 555 Timers

## A.C. Signal Sources

- Required for troubleshooting, designing of electronic circuits and systems
  - Indispensable tool in R&D of electronics and Communication engineering
- Desirable Properties**
- Low harmonic Content
  - Stable Operating frequency
  - Stable Output amplitude
  - Low noise


## Oscillator

- Basic element of all ac signal sources
- Generates repetitive waveform of fixed frequency and amplitude
- Oscillators are also used in
  - Superheterodyne receivers
  - Clock Pulse in digital circuits
  - Sweep units in TV sets, Oscilloscopes

## Diff. bet<sup>n</sup> Oscillator and Amplifier

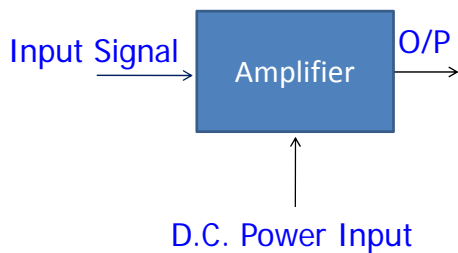
### Amplifier

- Output signal changes with the change in input signal



### Oscillator

- No input signal is required

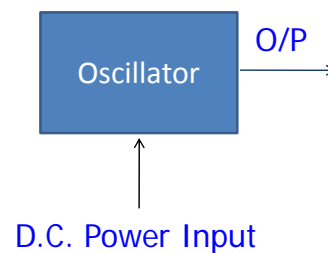

Lecture Slides on Oscillators

5

## Oscillators

- Oscillators obey law of conservation of energy
- Oscillators merely acts as energy converters
- Converts the unidirectional current drawn from a d.c. source of supply into alternating current of desired frequency
- Oscillators are also called inverters and are opposite to rectifiers
- In Instrumentation Oscillators are also known by different names such as function generators, test oscillators .....

Lecture Slides on Oscillators

6

## Oscillator Types

- Oscillators can be categorized according to
  - Type of component used (RC, LC, Crystal)
  - Frequency of Oscillation (AF, RF)
  - Type of waveform generated (Sinusoidal, Square Wave, Triangular Wave, Sawtooth Wave)

Lecture Slides on Oscillators

7

## Frequency Stability of Oscillator

- Measure of the oscillator's ability to maintain a constant frequency over as long interval of time as possible
  - Practically, there are some factors that affect the frequency stability of Oscillator
- Factors Affecting Frequency Stability**
- Circuit Components
    - Values of R, L and C changes with temperature
  - Transistor Parameters
    - Variation in temperature causes variation in transistor parameters

Lecture Slides on Oscillators

8


## Factors Affecting Frequency stability of an Oscillator (contd...)

- Supply Voltages
  - Variations in power supply
- Stray Capacitances
- Output Load
  - Variations of load causes a change in effective resistance
- Inter-element Capacitance

Lecture Slides on Oscillators

9

## Principle of Oscillator

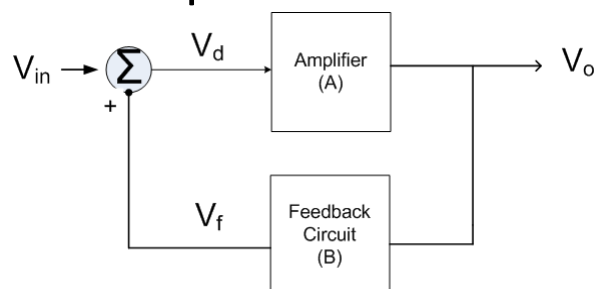


- An oscillator can be considered as a **feedback amplifier** in which part of the output is fed back to the input via a feedback circuit. If the signal is of **proper magnitude and phase**, the circuit produces alternating voltages or currents.

Lecture Slides on Oscillators

10
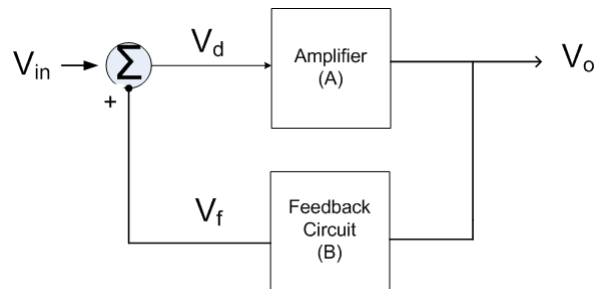
## Derivation of Voltage Gain in a Positive feedback circuit



- $V_d = V_f + V_{in}$
- $V_{in} = V_d - V_f$  .....i
- $V_o = AV_d$  .....ii
- $V_f = BV_o$  .....iii

Determine  $V_o/V_{in}$  in terms of A and B ?

## Derivation (continued.....)

### Equations

- $V_d = V_f + V_{in}$
- $V_{in} = V_d - V_f$  .....i
- $V_o = AV_d$  .....ii
- $V_f = BV_o$  .....iii

$$\frac{V_o}{V_{in}} = \frac{AV_d}{V_d - V_f} = \frac{AV_d}{V_d - BV_o} = \frac{A}{1 - AB} \left[ \text{since, } \frac{V_o}{V_d} = A \right]$$

## Barkhausen Criterion

- The overall voltage gain for a positive feedback amplifier is given as,

$$\frac{V_0}{V_{in}} = \frac{A}{1-AB}$$

- $V_{in}$  is zero for Oscillator
- i.e.  $1-AB=0$ , i.e.  $AB=1$
- This condition needs to be fulfilled for Sustained Oscillations and is called the Barkhausen Criterion

Lecture Slides on Oscillators

13

## Barkhausen Criterion (contd....)

- When  $AB=1$  is expressed in polar form,  
 $AB=1 \angle 0^\circ \text{ or } 360^\circ$
- The above equation gives two requirements for oscillations
  - i) The magnitude of  $AB$  must be equal to 1.
  - ii) The total phase shift of the loop gain  $AB$  must be equal to 0 or 360 degrees

Lecture Slides on Oscillators

14

## Oscillator Illustration

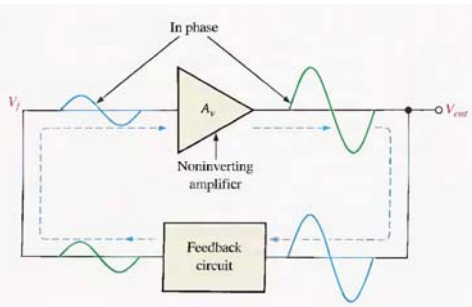


Fig.1 Oscillator Action

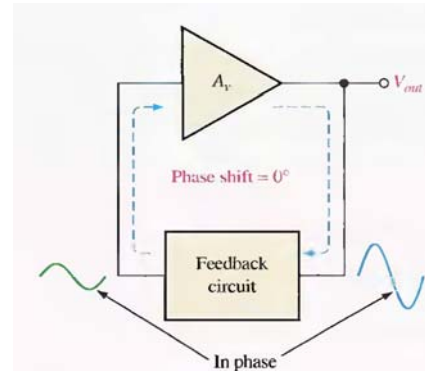


Fig.2 The phase shift around the loop is zero

## Questions ??

- If the oscillator is initially off and there is no output voltage then how does a feedback signal originate to start the positive feedback build up process?
- For those students who were absent during the last class email the answer to [coursekec@gmail.com](mailto:coursekec@gmail.com) and win bonus marks




## RC Oscillators

- Uses RC circuits to produce oscillations
- In the chapter we'll dealing with the following RC Oscillators
  - Wien Bridge Oscillator
  - Phase Shift Oscillator

## Wien Bridge Oscillator

- In any oscillator circuit, the total phase shift around the closed loop should be either zero or 360 degrees.
- In Wien Bridge oscillator amplifying as well as the frequency determining network both introduce zero phase shift.
- This is the basic principle of Wien Bridge Oscillator

## Wien Bridge.....

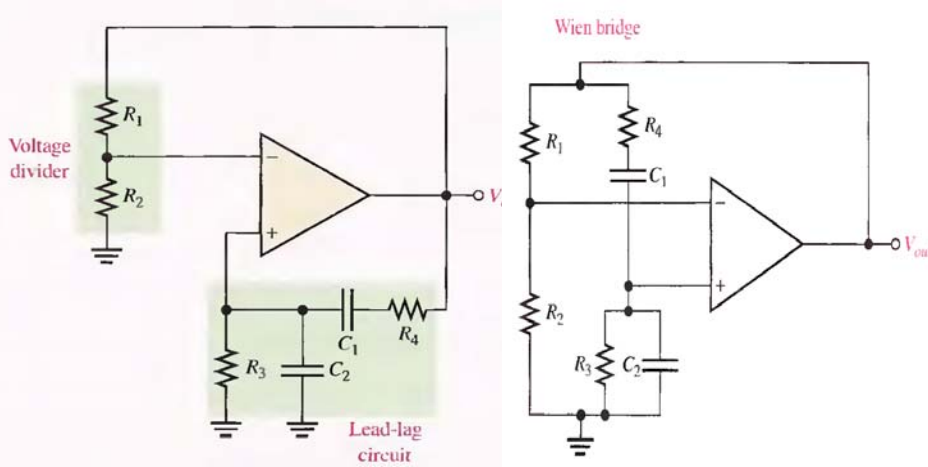

## Wien Bridge Oscillator Circuit

Lecture Slides on Oscillators

19

## Lead Lag Circuit

- It's a fundamental circuit in Wien Bridge Oscillator

Lecture Slides on Oscillators

20