

# CHAPTER 6 (OSCILLATORS) PHASE SHIFT OSCILLATORS

**Course Instructor (2EA)**

**AJAY KUMAR KADEL**

**ASSISTANT LECTURER (KEC, Kalimati)**

**Course Homepage**

**[www.courses.esmartdesign.com](http://www.courses.esmartdesign.com)**

1

## REMAINING PORTIONS

- Phase Shift Oscillator
- LC Oscillators
- Astable Multivibrators
- Square Wave Generators
- Triangular Wave Generators
- 555 Timer

## Phase Shift Oscillators Introduction

- At low frequencies (around 100 KhZ or less) combination of resistors are usually employed to determine frequency of oscillation
- Phase shift oscillator is a sinusoidal feedback oscillator
- Employs 3 resistors and 3 capacitors to determine the frequency of Oscillation

Lecture Slides on Oscillators part 2

3

## Circuit Diagram of Phase Shift Oscillator


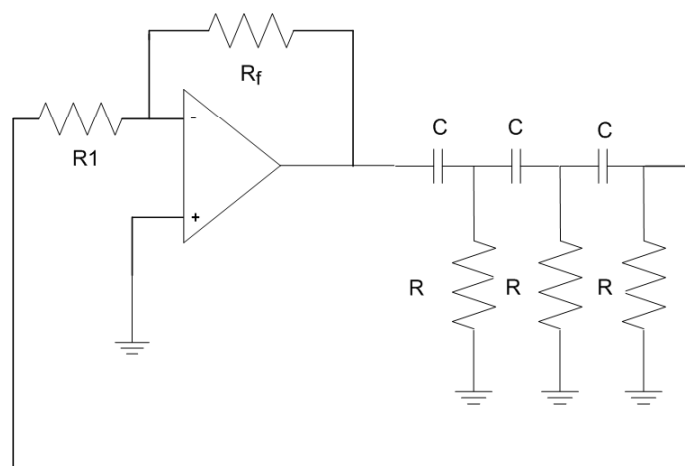


Fig. Phase Shift Oscillator

Lecture Slides on Oscillators part 2

4

## RC Phase-Shift Oscillator

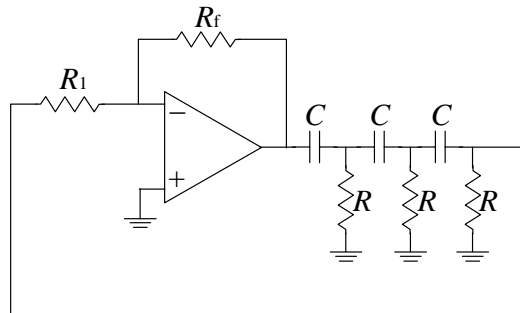

- Using an inverting amplifier
- The additional  $180^\circ$  phase shift is provided by an RC phase-shift network

5


Applying KVL to the phase-shift network, we have

$$\begin{aligned} V_1 &= I_1(R - jX_C) - I_2R \\ 0 &= -I_1R + I_2(2R - jX_C) - I_3R \\ 0 &= -I_2R + I_3(2R - jX_C) \end{aligned}$$

Solving for  $I_3$ , we get

$$I_3 = \frac{\begin{vmatrix} R - jX_C & -R & V_1 \\ -R & 2R - jX_C & 0 \\ 0 & -R & 0 \end{vmatrix}}{\begin{vmatrix} R - jX_C & -R & 0 \\ -R & 2R - jX_C & -R \\ 0 & -R & 2R - jX_C \end{vmatrix}}$$

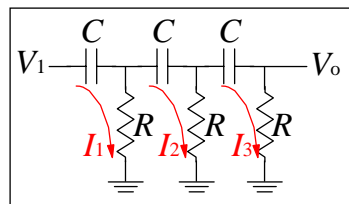Or 
$$I_3 = \frac{V_1 R^2}{(R - jX_C)[(2R - jX_C)^2 - R^2] - R^2(2R - jX_C)}$$



6

The output voltage,

$$V_o = I_3 R = \frac{V_1 R^3}{(R - jX_C)[(2R - jX_C)^2 - R^2] - R^2(2R - jX_C)}$$

Hence the transfer function of the phase-shift network is given by,

$$\beta = \frac{V_o}{V_1} = \frac{R^3}{(R^3 - 5RX_C^2) + j(X_C^3 - 6R^2X_C)}$$

For 180° phase shift, the imaginary part = 0, i.e.,

$$X_C^3 - 6R^2X_C = 0 \text{ or } X_C = 0 \text{ (Rejected)}$$

$$\Rightarrow X_C^2 = 6R^2$$

$$\omega = \frac{1}{\sqrt{6RC}}$$

and,

$$\beta = -\frac{1}{29}$$

Note: The -ve sign means the phase inversion from the voltage

7

## PHASE SHIFT OSCILLATORS USING BJT

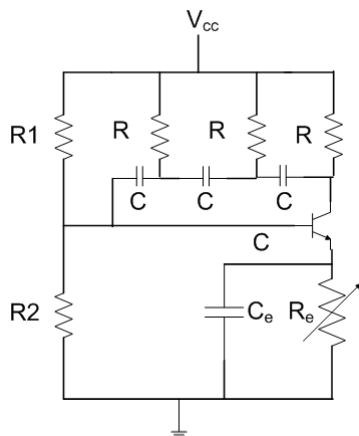


Fig.1 Phase shift Oscillator using BJT



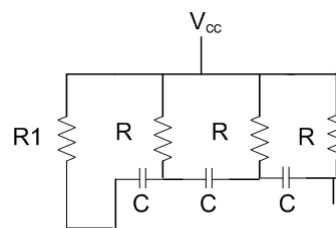


Fig.2 Dissecting the upper half

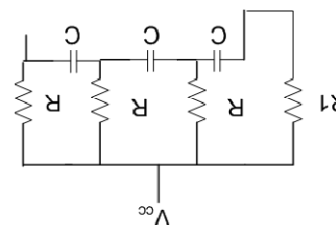


Rotating fig. 2 by 180 degrees

## Approximate Equivalent Circuit

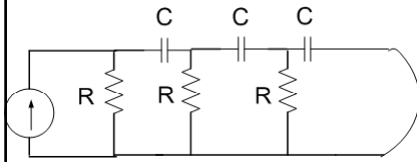

Derive  $i_4/i_1 = -1/29$

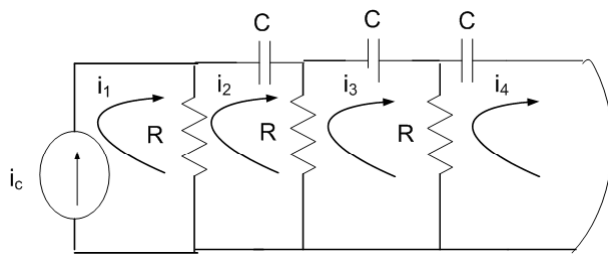

Lecture Slides on Oscillators part 2

9