

KATHMANDU ENGINEERING COLLEGE

Department of Electronics, Computer and Electrical Engineering

Tutorial Set No.1

ELECTRONIC CIRCUITS I

BEX Section A

Instructor: Ajay Kumar Kadel (AK)

Problem 1 (7 points)

Draw a circuit diagram of emitter unbypassed common emitter amplifier. Also find its input and output ac resistances. Also find its voltage gain.

Problem 2 (6 points)

Draw a basic circuit diagram to study the i_D - V_{DS} characteristics of a N-channel JFET. Also show the border line between triode and pinch off regions.

Problem 3 (2 points)

To use a transistor as an amplifier, why do you generally prefer common emitter (CE) configuration rather than common base (CB) configuration?

Problem 4 (6 points)

How does JFET behave for (i) small values of V_{DS} and (ii) for large values of V_{DS} ? Why is the input impedances of such devices high?

Problem 5 (4 points)

How does an E-MOSFET differ from DE-MOSFET?

Problem 6 (5 points)

Draw large and small signal equivalent circuit model of NPN BJT operating in active mode as voltage controlled current source.

Problem 7 (2 points)

Draw large and small signal equivalent circuit model of a PN junction diode.

Problem 8 (4 points)

How is depletion type MOSFET different from a JFET? Why is the input impedances of such devices high?

Problem 9 (8 points)

Define transconductance g_m for a JFET and show how it depends upon the dc bias point. Compare BJT with MOSFET.

Problem 10 (8 points)

Draw a common emitter amplifier circuit using npn transistor with two emitter resistances (R_{E1} is NOT bypassed while R_{E2} is bypassed using CE). Find the voltage gain of this circuit. Explain how input resistance can be increased in the common emitter amplifier?