

KATHMANDU ENGINEERING COLLEGE  
Department of Electronics, Computer and Electrical Engineering

Tutorial Set No.2

**ELECTRONIC CIRCUITS I**

BEX Section A

Instructor: Ajay Kumar Kadel

**Deadline: Falgun 5, Monday (2:00 PM)**

---

- *Please promptly turn in your assignments. 10 % of your marks from this assignment will be deducted in case of late submission.*
  - *Please try to do the problems yourself since this course is best learned through problem solving.*
- 

**Problem 1 (7 points)**

Draw the block diagram of an operational amplifier and describe each block.

**Problem 2 (5 points)**

Draw a circuit diagram of widlar current source which supplies 10  $\mu\text{A}$  from a reference source current of 1mA and 0.7V of bias.

**Problem 3 (6 points)**

Draw a differential amplifier which uses active load. Also find its output voltage if the differential input voltage is " $v_{id}$ ".

**Problem 4 (10 points)**

Describe how a simple current mirror circuit produces the output current which is a mirror of its input reference current. Give two reasons for the output current  $I_0$  of a simple current mirror not being exactly equal to the reference current  $I_{ref}$ .

**Problem 5(4 points)**

Explain how a number of constant currents are generated by using current steering circuits for biasing various circuits in IC?

**Problem 6 (7 points)**

Define the input and output resistance of a differential amplifier. Show that the input resistance  $R_i$  of a dual input balanced output differential amplifier is equal to  $2\beta r_e$ .

**Problem 7 (5 points)**

What are the benefits of Widlar current source as compared to a simple current source?

**Problem 8 (4 points)**

Draw a circuit diagram of a current mirror whose output is one-half the reference current **without** using widlar current source.

**Problem 9 (10 points)**

Draw a Widlar current source and compare it with simple current mirror. Derive an equation for the output resistance of Widlar current source.

**Problem 10 (6 points)**

Prove that a differential amplifier amplifies the difference between two input signals. Draw the input and output waveforms of the dual input, balanced output differential amplifier.

**Problem 11 (8 points)**

For the dual input, balanced output differential amplifier (i) determine the output voltage if  $V_{in1}=50\text{mv}$  peak to peak at 1 KHZ and  $V_{in2}=20\text{mv}$  peak to peak at 1 KHZ. Assume voltage gain=86. (ii) What is the maximum peak to peak output voltage without clipping? Assume the current flowing through each collector is 1 mA.

**Problem 12 (2 points)**

Explain why open loop configurations of operational amplifiers aren't used in linear applications.

**Problem 13 (2 points)**

Sketch the output stage (dc level shifting) of any two op-amp circuit.

**Problem 14 (5 points)**

Explain any two d.c. level shifting circuits of op-amp.

**Problem 15 (5 points)**

Compare the voltage gain and output resistance of differential amplifier with active load and passive load ( $R_c$ ).

**Problem 16 (9 points)**

Draw the circuit diagram and compare the output resistances of the following current mirrors

- Simple current mirror
- Improved current mirror
- Wilson current mirror

**Problem 17 (5 points)**

Compare the voltage gain and output resistance of differential amplifier with active load and passive load ( $R_c$ ).

**Problem 18 (2 points)**

Explain why current mirrors are required in integrated circuit fabrication?

**Problem 19 (2 points)**

Explain why level shifting stage is required in operational amplifier?

**Problem 20 (8 points)**

Find the values of  $R_1$ ,  $R_2$ ,  $R_3$  and  $R_4$  in the given circuit of fig. P.20. Given data are

$$V_{BE} = 0.7\text{V when } I_C = 1\text{mA}$$

$$\eta = 1$$

$$I_{ref} = (\text{your roll number}) \mu\text{A}$$

$$I_{01} = (0.25 \times \text{your roll number}) \mu\text{A}$$

$$I_{02} = (0.5 \times \text{your roll number}) \mu\text{A}$$

$$I_{03} = (0.75 \times \text{your roll number}) \mu\text{A}$$

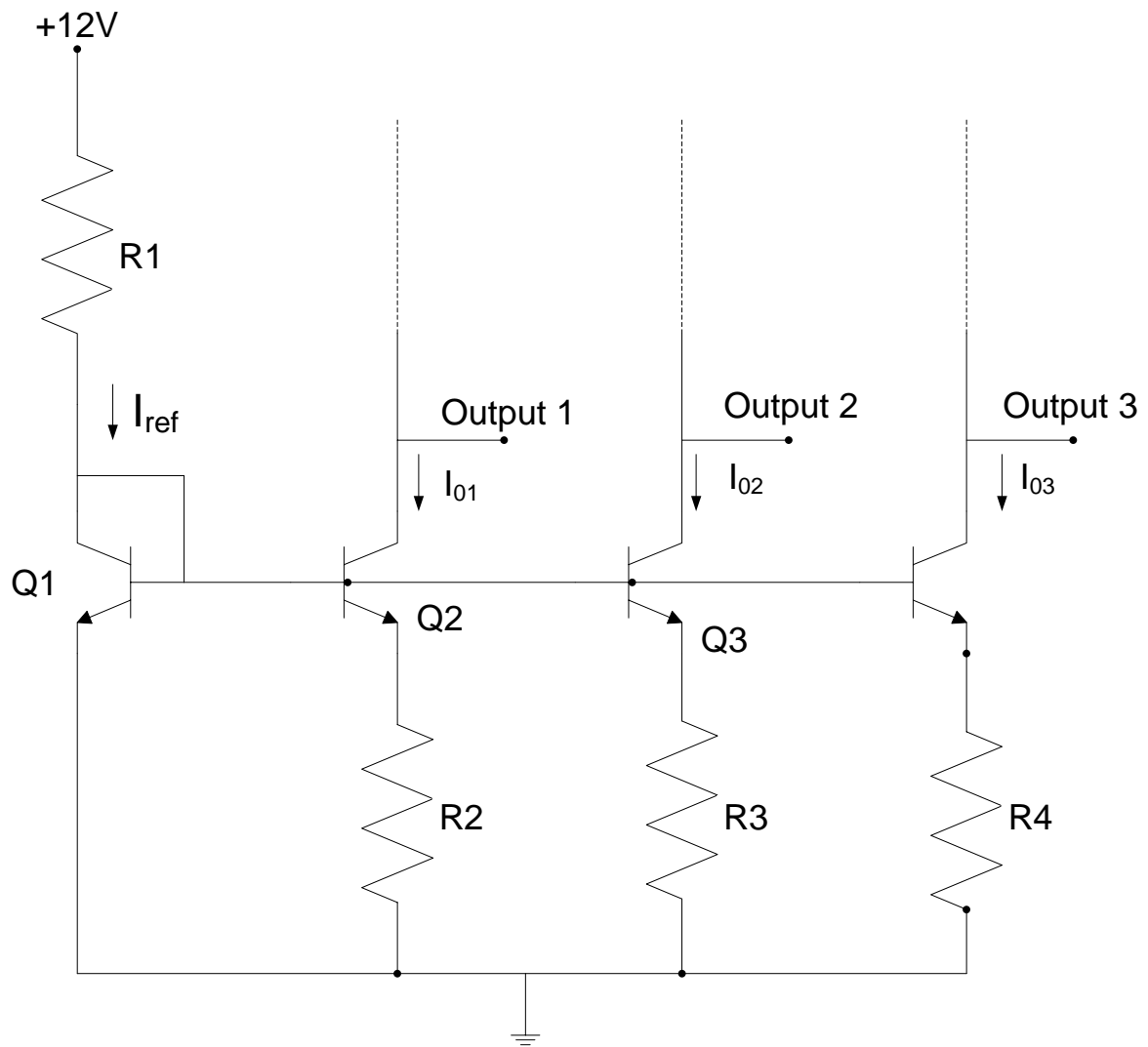


Fig. P.20